

Designing with VHDL

Designing with VHDL

- Overview of the Hardware Description Languages (HDL)
- VHDL for synthesis
 - Signals, types, vectors, hierarchy, attributes
 - Combinational circuits – concurrent vs. sequential assignments
 - Examples
 - Mathematical operations, packages
 - Sequential circuits – DFFs and latches
 - More examples
 - State machines
 - Error protection and error correction

Overview HDL – ABEL, AHDL, Verilog

- ABEL
 - Originally developed for SPLDs and still in use for SPLDs
 - Now owned by Xilinx
- AHDL
 - Developed by Altera, still used in Altera library components
 - Syntax similar to Ada
- Verilog HDL
 - Together with VHDL the standard HDL now
 - Syntax similar to C
- Other → SystemC, SystemVerilog, Verilog-AMS

VHDL

- VHDL = VHSIC Hardware Description Language
 - VHSIC = Very High Speed Integrated Circuit
- Developed on the basis of **ADA** with the support of the USA militaries, in order to help when making **documentation** of the digital circuits
- The next natural step is to use it for **simulation** of digital circuits
- And the last very important step is to use it for **synthesis** of digital circuits
- Versions: 1987, 1993, 2000, 2002 and 2008
- Together with **Verilog** is the mostly used language for development of digital circuits
- Extensions for simulations of analogue circuits


Structure of an **entity** in VHDL - example

```
LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;
```

```
entity a2of3 is
port (a0  : in  std_logic;
      a1  : in  std_logic;
      a2  : in  std_logic;
      y   : out std_logic);
end a2of3;
```

input ports

output port

 

```
architecture a of a2of3 is
signal g0, g1, g2 : std_logic;
```


```
begin
  g0 <= a0 and a1;
  g1 <= a1 and a2;
  g2 <= a2 and a0;
  y  <= g0 or g1 or g2;
end;
```

internal signals

the order of the assignments here is **not** important!

VHDL is not case-sensitive!

 Recommendation: 1 file – 1 entity
filename = name of the entity



Structure of an **entity** in VHDL

entity
port
in out
inout
buffer
architecture
signal

```
LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;
```

} + other library declarations, this is the standard minimum

```
entity <entity_name> is
port (
    <port_name>    : <in|out|inout|buffer> <signal_type>;
    ...
    <port_name>    : <in|out|inout|buffer> <signal_type>;
end <entity_name>;
```

port type

```
architecture <arch_name> of <entity_name> is
    ...
    signal <internal_signal> : <signal_type>;
    ...
```

+ optional **type** and **constant** declarations

```
begin
    -- comment to the end of the line
    ...
end [<arch_name>];
```

Unlike C and Verilog, VHDL is not case-sensitive!

/* block comment
in VHDL-2008 */

Instantiation of sub-blocks

```
LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;
```

```
entity fadd_top is
port (
  cin    : in  std_logic;
  a      : in  std_logic;
  b      : in  std_logic;
  cout   : out std_logic;
  s      : out std_logic);
end fadd_top;
```

```
architecture struct of fadd_top is
-- component declarations
component xor3 is
port (a0 : in  std_logic;
      a1 : in  std_logic;
      a2 : in  std_logic;
      y  : out std_logic);
end component;
```

```
component a2of3 is
port (a0 : in  std_logic;
      a1 : in  std_logic;
      a2 : in  std_logic;
      y  : out std_logic);
end component;
```

declare the
"pinout" of the
used
components

known as **STRUCTURAL** description


begin component name

```
sum: xor3
port map(
  a0 => a,
  a1 => b,
  a2 => cin,
  y  => s);


carr: a2of3
port map(
  a0 => a,
  a1 => b,
  a2 => cin,
  y  => cout);
end;
```

label

y <= a0 xor a1 xor a2;

 

Synthesis + techn. mapping

 


Instantiation – port-signal mapping

```
carr: a2of3
port map(
  a0 => a,
  a1 => b,
  a2 => cin,
  y  => cout);
```

```
carr: a2of3
port map(
  a0 => a,
  a2 => cin,
  a1 => b,
  y  => cout);
```

swapping of the
pairs is not
important

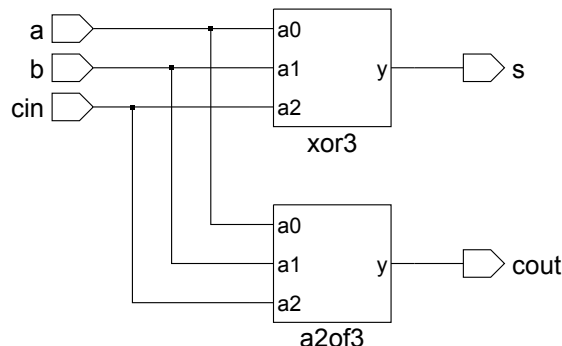


There is a shorter way to connect the ports of the component to the signals, shown to the right. **Not recommended**, as in this case the mapping relies on the correct order!

```
carr: a2of3
port map(a, b, cin, cout);
```


a wrong order of the signals here will change the circuit!!!

```
carr: a2of3
port map(a, cin, b, cout);
```

b and cin are swapped

 

Port-signal mapping – how to remember

 

Types of data in VHDL(1)

- **time** (**fs**, **ps**, **ns**, **us**, **ms**, **sec**, **min**, **hr**)
 - 1 ns, 20 ms, 5.2 us
- **real** (**-1e38**..**+1e38**)
- **integer** (**-(2³¹-1)** .. **2³¹-1**) with predefined subtypes **natural** (**≥0**) and **positive** (**>0**)

```
signal counter : Integer;
```

```
signal timer   : Natural;
```

- **boolean** has two possible values **FALSE** and **TRUE**
 - Not intended for electrical signals!
 - Typically used when checking some conditions, like

```
if a = b then -- equal
if a /= b then -- not equal
if a > b then -- larger
if a < b then -- smaller
if a <= b then -- smaller or equal
if a >= b then -- larger or equal
```


For other examples see
"Working with vectors" and
"Signal attributes"

↖ the result of the comparison is a **boolean**

Types of data in VHDL(2)


- **bit** has two possible values '0' and '1'
 - These two values are not enough to model real hardware!
- **std_(u)logic** to the '0' and '1', introduced 7 additional values for tri-stated ('Z'), unknown ('X'), weak 0 ('L'), weak 1 ('H'), weak unknown ('W'), uninitialized ('U') and don't care ('-')

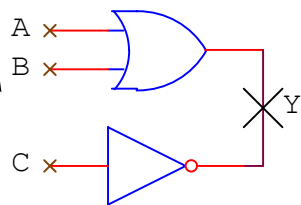This is allowed only when using **std_logic** but not **std_u logic** or **bit**!



```
Y <= not C;
Y <= A or B;
```

 Example for pull-up (weak 1) and tri-stated outputs, **std_logic** is required




```
Y <= 'H' ;
```

```
Y <= A when OE_A='1' else 'Z' ;
```

```
Y <= B when OE_B='1' else 'Z' ;
```

The std_logic type

 ... is a resolved version of **std_ulogic**, this means there is a method to resolve the conflicts when one signal has multiple drivers




	U	X	0	1	Z	W	L	H	-		
'U'	'U'	'U'	'U'	'U'	'U'	'U'	'U'	'U'	'U'	U	Uninitialized
'U'	'X'	'X'	'X'	'X'	'X'	'X'	'X'	'X'	'X'	X	Forcing Unknown
'U'	'X'	'0'	'0'	'X'	'0'	'0'	'0'	'0'	'X'	0	Forcing 0
'U'	'X'	'X'	'1'	'1'	'1'	'1'	'1'	'1'	'X'	1	Forcing 1
'U'	'X'	'0'	'1'	'Z'	'W'	'L'	'H'	'X'	'X'	Z	High Impedance
'U'	'X'	'0'	'1'	'W'	'W'	'W'	'W'	'X'	'X'	W	Weak Unknown
'U'	'X'	'0'	'1'	'L'	'W'	'L'	'W'	'X'	'X'	L	Weak 0
'U'	'X'	'0'	'1'	'H'	'W'	'W'	'H'	'X'	'X'	H	Weak 1
'U'	'X'	'X'	'X'	'X'	'X'	'X'	'X'	'X'	'X'	-	Don't care

Tri-state and bidirectional ports

```
entity triout is
port (outp : out std_logic;
      dout : in  std_logic;
      oe   : in  std_logic);
end triout;
architecture b of triout is
begin
  outp <= dout when oe='1' else 'Z';
end;
```


compare!

```
entity bidir is
port (iopin : inout std_logic;
      din   : out  std_logic;
      dout  : in   std_logic;
      oe    : in   std_logic);
end bidir;
...
with iopin select
din   <= '0' when '0' | 'L',
        '1' when '1' | 'H',
        'X' when others;
with oe select
iopin <= dout when '1',
        'Z'   when '0',
        'X'   when others;
end;
```

 

When using tri-stated buses driven by multiple drivers:

 - Be sure that only one driver is active at the same time
- Insert turn-around cycles when changing the driver of the line with all drivers turned off



- Internal tri-state lines are typically not supported for FPGAs, some tools convert them to multiplexers

Buffer ports

A signal of the mode **out** can not be used back as input in the entity. There are two solutions for this problem, either *using the **buffer** mode of the entity port:*


```
port (
  a      : in    std_logic;
  b      : in    std_logic;
  c      : in    std_logic;
  ya     : buffer std_logic;
  yao    : out   std_logic);
```

```
...
begin
  ya <= a and b;
  yao <= ya or c;
```

buffer is allowed to be read back but **out** not!

buffer ?

Not recommended!

 


the standard solution

```
port (
  a      : in    std_logic;
  b      : in    std_logic;
  c      : in    std_logic;
  ya     : out   std_logic;
  yao    : out   std_logic);
```

```
...
signal ya_i : std_logic;
begin
  ya_i <= a and b;
  yao <= ya_i or c;
  ya <= ya_i;
```


use additional internal signal

 

If the port **ya** is connected to another driver (driving '1' in this simulation), the internal signal **ya_i** is not affected!

with ... select
others
' - '

 
Example for don't care ' - ' with a multiplexer 3:1




SEL	Y
0	I0
1	I1
2	I2
3	?

What is the benefit of ' - ' ?

 - automatic choice of the best value
- undefined output when the input **SEL** is unexpected in the functional simulation


 
```
with SEL select
Y <= I2 when "10",
    I1 when "01",
    I0 when others;
```



```
with SEL select
Y <= I2 when "10",
    I1 when "01",
    I0 when "00",
    ' - ' when others;
```



More complex data types

- **Array**

- predefined in IEEE.STD_LOGIC_1164, e.g. `std_logic_vector(3 downto 0);`
`subtype reg_data is std_logic_vector(31 downto 0);`
`type mem_array is array(0 to 63) of reg_data;`

the direction
of the index

- **Enumerated**

- Used mainly to describe state machines
`type state_type is (idle, run, stop, finish);`

- **Record**

```
type lvds_t is record a, b : std_logic; end record;
type ni_port_out_t is record
    ctrl      : lvds_t;
    clk       : lvds_t;
    pretrig   : lvds_t;
end record;
```

records in record
is allowed

```
signal niP4 : ni_port_out_t;
signal myclk : lvds_t;
```

...

```
myclk.a <= clk;
myclk.b <= not clk;
niP4.clk <= myclk;
```

access to the elements of the
record like in C and Pascal

Generic

- **Generic** is a parameter of the **entity**, which is known at the compilation time
- The same **entity** can be instantiated many times with different values of the **generic(s)**
- Typically the generics are of type **integer**, **boolean** or **time**

```
entity mux2lnbit is
```

```
generic(N : Integer := 4; tdel : time := 2 ns);
```


```
port(A0, A1 : in std_logic_vector(N-1 downto 0);  
      SEL   : in std_logic;  
      Y     : out std_logic_vector(N-1 downto 0));  
end entity;
```

this is only the **default** value, used when no "**generic map**" found (next slide)

The **default** value is the actual value used when the entity is the **top** of the design

Generic map - example
 
```
entity mux41 is
port(A0, A1 : in  std_logic_vector(5 downto 0);
      A2, A3 : in  std_logic_vector(7 downto 0);
      SEL    : in  std_logic_vector(1 downto 0);
      Y      : out std_logic_vector(7 downto 0));
end mux41;
```



```
architecture struct of mux41 is
```

```
component mux21nbit is
```

```
generic(N : Integer := 4; tdel : time := 2 ns);
```

```
port(A0, A1 : in  std_logic_vector(N-1 downto 0);
```

```
      SEL    : in  std_logic;
```

```
      Y      : out std_logic_vector(N-1 downto 0));
```

Component declaration

```
end component;
```

```
signal y01 : std_logic_vector(5 downto 0);
```

```
signal y23 : std_logic_vector(7 downto 0);
```

```
begin
```

```
m01: mux21nbit
```

```
generic map(N => 6)
```

```
port map(A0 => A0, A1 => A1,
          SEL => SEL(0), Y => y01);
```

```
m23: mux21nbit
```

```
generic map(N => 8)
```


```
port map(A0 => A2, A1 => A3,
          SEL => SEL(0), Y => y23);
```

```
my: mux21nbit
```

```
generic map(N => 8)
```

```
port map(A0 => "00" & y01, A1 => y23, SEL => SEL(1), Y => Y);
```

extend y01

 

Overwrite the default value of the generic N


Working with vectors - aggregates

```

a : in  std_logic_vector(2 downto 0);
b : in  std_logic_vector(2 downto 0);
c : out std_logic_vector(5 downto 0);
d : out std_logic_vector(5 downto 0);
e : out std_logic_vector(5 downto 0);
f : out std_logic_vector(2 downto 0);

```

c <= a & b;

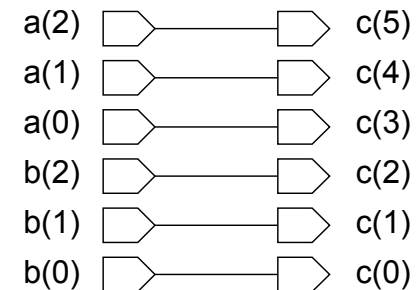


leftmost in e index


```

e <= (a(0), b(1), 0 => '1', others => '0');


```

 

(f(0), f(2), f(1)) <= a;

 

d <= a(2) & b(2) & x"C";

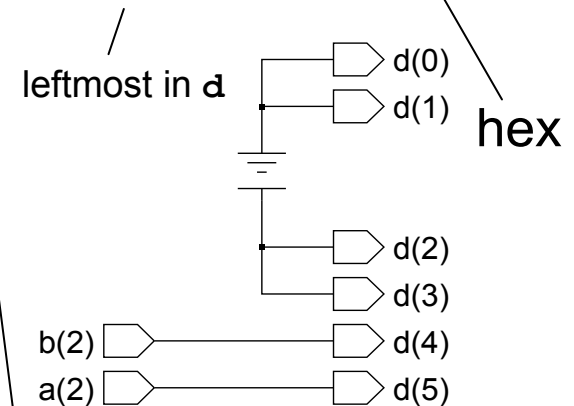

Working with vectors - multidimensional

- Two-dimensional vectors are typically not supported by the most software tools
- One simple way is to declare a new type as vector of vectors:

```
subtype my_data is std_logic_vector(15 downto 0);  
type my_array is array(0 to 7) of my_data;
```

OR simply

```
type my_array is array(0 to 7) of  
    std_logic_vector(15 downto 0);
```

Working with vectors – attributes

`generic (N : Natural := 4);` ————— use **generic** to set the size

```
port (
  a : in  std_logic_vector(2 to N+1);
  c : out std_logic_vector(N-1 downto 0);
  d : out std_logic_vector(N-1 downto 0) );
...
gn: for i in 0 to c'length-1 generate
      c(c'low + i) <= a(a'low + i);
    end generate;
d <= a;
```

```

a(2) —> c(0) —> d(3)
a(3) —> c(1) —> d(2)
a(4) —> c(2) —> d(1)
a(5) —> c(3) —> d(0)
```

Be careful when mixing arrays
with different directions
(**to** ↔ **downto**)!

Use the predefined attributes
to access different parameters
of the array

a'length, c'length	N
a'low, a'left	2
a'high, a'right	N+1
c'low, c'right	0
c'left, c'high	N-1
a'ascending	TRUE
c'ascending	FALSE
a'range	2 to N+1
c'range	N-1 downto 0

for ... generate

...can be used to repeat some assignments or instantiations

label

`<label>: for i in <range> generate`
...
`end generate;`

`i` is integer, but is defined only inside the generate and don't need to be declared!

the range is either:
`<low> to <high>`
or
`<high> downto <low>`

integer constants at the compilation time!

The restrictions are the same as for

`if .. generate .. end generate`

Used in several examples later

Conditional code – if ... generate

In many programming languages (e.g. in C with **#define ... #ifdef ... #endif**) one can compile some parts of the source code depending on some condition. In VHDL one can use for the same purpose a **boolean generic** parameter and **if ... generate ... end generate**.

This is useful to configure the entity, instead of creating many variants as different entities.

This construct can not be used so freely as the **#ifdef** in C.

The usage is restricted to the **architecture** part of the **entity**, but outside processes. So one can include or exclude complete concurrent assignments or processes or entity instantiations.

```
...
generic(opeipe : Boolean := true);
... label
op1: if opeipe generate
  oreg: dff_array
  generic map(N => datout'length)
  port map(
    clk => clk,
    d   => dat_m,
    q   => datout);
end generate;
label
op0: if not opeipe generate
  datout <= dat_m;
end generate;
else generate
VHDL-2008
```

Output with/without register, depending on the **generic** parameter **opeipe**

VHDL-2008: **else generate, elsif generate, case <const> generate**

Constants

- Can be declared in the architecture part together with the signals or in the packages

```
constant <constant_name> : <constant_type> := <value>;
```

```
constant Nbits : Integer := 8;
```

```
constant Nwords : Integer := 6;
```

Put the sizes of the
vectors in constants

```
subtype my_word is std_logic_vector(Nbits-1 downto 0);
```

```
type my_array is array(0 to Nwords-1) of my_word;
```

```
constant all1 : my_word := (others => '1');
```

```
constant all0 : my_word := (others => '0');
```

```
constant arr_ini : my_array := (all0, all1, x"01", x"12",  
                                others => "10101111");
```

hex

0x00	0
0xFF	
0x01	
0x12	
0xAF	
0xAF	5

```
constant Tco : time := 5 ns;
```

```
constant Tsetup : time := 2 ns;
```

```
constant Thold : time := 1 ns;
```




Constants of type **time**

Combinational circuits in VHDL(1)

or
nor
and
nand
xor
xnor
not

- Using simple assignments and Boolean expressions:

```
y <= (a or b) and not c;  
y <= a or b and not c; -- invalid!  
y <= a and b or not c; -- invalid!  
y <= a and b and not c;  
y <= a or b or not c;  
y <= (a nor b) nor c;  
y <= a nor b nor c; -- invalid!  
y <= (a nand b) nand c; -- invalid!  
y <= a nand b nand c; -- invalid!  
y <= a xor b and c; -- invalid!  
y <= (a xor b) and c;  
y <= a xor b xor c;  
y <= a xnor b xnor c; -- invalid!  
y <= a xor b xnor c;
```

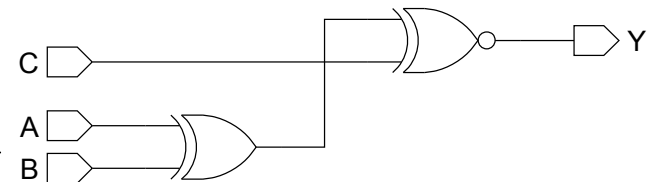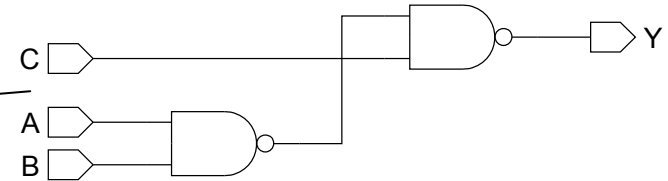 

Use brackets when more than 2 operands and different operations!

Combinational circuits in VHDL(2)

when ... else
with ... select
process
if ... then ...

- Using Boolean equation + a condition: **conditional signal assignment**

```
y <= (a or b) when c = '0' else '0';
```
- Like a table, giving the output for all possible inputs: **selected signal assignment**

```
with a & b & c select  
  y <= '1' when "110" | "100" | "010",  
  '0' when others;
```
- Using **process** – sequential code, like in a normal programming language

```
process (a, b, c) ← sensitivity list  
begin  
  y <= '0';  
  if a = '1' or b = '1' then y <= '1'; end if;  
  if c = '1' then y <= '0'; end if; ← The last value assigned will be stored in y  
end process;
```


Caution: in all cases the synthesis generates logic working in parallel! Only the compiler/simulator “executes” sequentially the process to “understand” what do we require from it!

Concurrent assignments

- In the real hardware all gates work in parallel
- In VHDL we can use statements which are executed in parallel (concurrent in time), like

```
a_or_b <= a or b;  
y <= a_or_b when c = '0' else '0';  
with d & y select  
q <= '1' when "10" | "01",  
  '0' when others;
```

 The order of the assignments in the VHDL code here is NOT important!



known as **DATAFLOW** description

Normally we DON'T assign more than ONCE a value to a signal in the entity


A change in any signal propagates to all other signals depending on it, the assignments are continuously active!

Sequential assignments for combinational logic

- We can use assignments which are executed sequentially in a **process**

```
process (a, b, c)
begin
    y <= '0';
    if a = '1' or b = '1' then y <= '1'; end if;
    if c = '1' then y <= '0'; end if;
end process;
```

 The **process** doesn't run continuously! It will be started only after change (**event**) on any signal in its **sensitivity list**



known as **BEHAVIOUR** description

After an event in **a**, **b** or **c**:

- 1) new value '0' is scheduled for **y**, but **y** still has its old value
- 2) if **a** or **b** are '1', the new scheduled value of **y** is changed to '1'
- 3) if **c** is '1', the scheduled value of **y** is changed to '0'
- 4) at the end of the **process** the scheduled value is assigned to **y**
- 5) as **y** is not on the sensitivity list, the **process** is suspended until the next event on **a**, **b** or **c**, and **y** preserves its new value

All this happens within the same simulation *time*!

The order of the assignments in the process

... is very important!

```
process (a, b, c)
```

```
begin
```

```
1  y <= '0';
```

```
2  if a = '1' or b = '1' then y <= '1'; end if;
```

```
3  if c = '1' then y <= '0'; end if;
```

```
end process;
```

```
process (all) -- VHDL-2008
```

The 6 possible
permutations in
the process

are
equivalent to

the following concurrent
assignments

1-2-3

2-3-1, 3-2-1, 2-1-3

1-3-2, 3-1-2


```
y <= (a or b) and not c;
```

```
y <= '0';
```

```
y <= a or b;
```

Sequential assignments for combinational logic synthesis

 - Think about the **process** as a way to describe the reaction of the combination circuit on events on its inputs




The compiler just calculates the truth table of the circuit in order to synthesise the logic!

The real hardware consists only of GATES!

The outputs of the combinational circuit should depend only on the **present** values of the inputs but **not** on the **past** → this implies that all outputs of the **process** **must** get some value assigned after **any** activation of the **process**!

Simulation deltas
 
```
process(a, b)
begin
    w <= not y;
    y <= a or b;
end process;
```



```
process(a, b, y)
begin
    w <= not y;
    y <= a or b;
end process;
```

ns	delta	a	b	y	w
0	0	1	0	U	U
0	1	1	0	1	U
20	1	0	0	1	U
20	2	0	0	0	0
40	1	1	1	0	0
40	2	1	1	1	1
60	1	0	1	1	1
60	2	0	1	1	0
80	1	1	0	1	0

```
process
begin
    a <= '1'; b <= '0';
    wait for 20 ns;
    a <= '0'; b <= '0';
    wait for 20 ns;
    a <= '1'; b <= '1';
    wait for 20 ns;
    a <= '0'; b <= '1';
    wait for 20 ns;
    a <= '1'; b <= '0';
    wait;
end process;
```

ns	delta	a	b	y	w
0	0	1	0	U	U
0	1	1	0	1	U
0	2	1	0	1	0
20	1	0	0	1	0
20	2	0	0	0	0
20	3	0	0	0	1
40	1	1	1	0	1
40	2	1	1	1	1
40	3	1	1	1	0
60	1	0	1	1	0
80	1	1	0	1	0

Gating of a vector

```
...
generic (N : Natural := 4);
port (
  a : in  std_logic_vector(N-1 downto 0);
  g : in  std_logic;
  y : out std_logic_vector(N-1 downto 0) );
end for_gen;
architecture ... of for_gen is
  signal tmp : std_logic_vector(a'range);
begin
```

① `y <= a and g;`

② `tmp <= (others => g);`
`y <= a and tmp;`

and between two
`std_logic_vectors`
of the same size

④ `gn: for i in a'range generate`
 `y(i) <= a(i) and g;`
 `end generate;`


label

VHDL-2008

many possible
codes

③ `y <= a when g='1' else (others => '0');`

 ⑤ `process(a,g)`
begin
 if g='1' then y <= a;
 else y <= (others => '0'); end if;
end process;



```

when ... else
    process
        if ... then ...
    elsif ... end if

```

Priority encoder

1

```

irq_no <= "11" when IRQ(3) = '1' else
        "10" when IRQ(2) = '1' else
        "01" when IRQ(1) = '1' else
        "00" when IRQ(0) = '1' else
        "--";


```

```

valid <= IRQ(0) or IRQ(1) or IRQ(2) or IRQ(3);

```

1-st method
(dataflow style)

 

2

```

pri: process (IRQ)
begin

```


```

    valid <= '1';
    irq_no <= "--";
    if      (IRQ(3) = '1') then irq_no <= "11";
    elsif   (IRQ(2) = '1') then irq_no <= "10";
    elsif   (IRQ(1) = '1') then irq_no <= "01";
    elsif   (IRQ(0) = '1') then irq_no <= "00";
    else    valid <= '0';
    end if;
end process;

```

2-nd method,
using a **process**
(behaviour style)

 Priority encoder – synthesis for 3 different technologies



Priority logic constructs

- Concurrent assignments – **when ... else ...**

same type **Boolean**

```
<signal> <= <expression_1> when <condition_1> else  
                 <expression_2> when <condition_2> else  
                 ...  
                 <expression_n>;
```

- In a **process** this is equivalent to the following
if ... then ... elsif ... else

process(...) put in the sensitivity list all signals read in the process!

```
begin  
  if        <condition_1> then signal <= <expression_1>;  
  elsif <condition_2> then signal <= <expression_2>;  
  ...  
  else <signal> <= <expression_n>;  
  end if;  
end process;
```

if-then-else can be used only in a **process**! It can be used for more than an assignment to a single signal

```

with ... select
    process
    case ... is ...
    when ... end case

```

Multiplexer

Two equivalent descriptions, here because of the different length of `status`, `cfg1`, `cfg2`, `cfg3`, the `process` description is nicer

①

```

with SEL select
Y <= "00000" & status when "00", -- 3 bits
    "00"      & cfg1  when "01", -- 6 bits
    "0000"    & cfg2  when "10", -- 4 bits
    "000000"  & cfg3  when "11", -- 2 bits
    (others => 'X')   when others;

```


②

```

process(status, cfg1, cfg2, cfg3, SEL)
begin
    Y <= (others => '0');
    case SEL is
    when "00" => Y(status'range) <= status;
    when "01" => Y(cfg1'range)   <= cfg1;
    when "10" => Y(cfg2'range)   <= cfg2;
    when "11" => Y(cfg3'range)   <= cfg3;
    when others => Y <= (others => 'X');
    end case;
end process;

```

1-st method (dataflow style)

 

2-nd method,
using a `process`
(behaviour style)

Demultiplexer

1

```
with SEL select
  Y <= I & "000"      when "11",
    '0' & I & "00"    when "10",
    "00" & I & '0'    when "01",
    "000" & I         when "00",
    (others => 'X')    when others;
```

2

```
process(I, SEL)
begin
  Y <= (others => '0');
  case SEL is
    when "00" => Y(0) <= I;
    when "01" => Y(1) <= I;
    when "10" => Y(2) <= I;
    when "11" => Y(3) <= I;
    when others => Y <= (others => 'X');
  end case;
end process;
```


3

```
process(I, SEL)
begin
  Y <= (others => '0');
  Y(conv_integer(SEL)) <= I;
end process;
```

1-st and 2-nd method:

- not scalable

 + in case of undefined **SEL** input,
all outputs are 'x'



3-rd method

+ compact, scalable

- in case of undefined **SEL**
input, **Y (0)** will be
activated!

Non-priority selection logic

- Concurrent assignments – **with ... select ... when**

```
with <signal_s> select
  <signal> <= <expression_1> when <case_1>,
  <expression_2> when <case_2>,
  ...
  <expression_n> when others;
```

constants of the same
type as <signal_s>

- In a **process** this is equivalent to the following:

case can be used only
in a **process**! It can be
used for more than an
assignment to a single
signal

```
process(<signal_s>, ...)
begin
  case <signal_s> is
    when <case_1> => <signal> <= <expression_1>;
    when <case_2> => <signal> <= <expression_2>;
    ...
    when others    => <signal> <= <expression_n>;
  end case;
end process;
```

In both cases **all** possible values of the <signal_s> must be specified (<case_1>, <case_2>...) exactly once, either explicitly or only some of them + the rest using **when others**!

Type conversions

- VHDL is strictly typed language
- Even mixing of **bit** and **std_logic** is not directly possible, but normally this is not necessary
- An array of **bit** (or **std_logic**) can not be directly used as integer number, but it is frequently used to hold integer numbers
- A conversion function (own or from some library) should be used

```
USE IEEE.STD_LOGIC_ARITH.all;
USE IEEE.STD_LOGIC_UNSIGNED.all;
...
signal data11bits : std_logic_vector(10 downto 0);
signal tsti : Integer range 0 to 2047;
...
data11bits <= conv_std_logic_vector(2046,11); --> "11111111110"
tsti <= conv_integer(data11bits); --> 2046
-- The same constant can be loaded in data11bits with:
data11bits <= (0 => '0', others => '1');
```

integer value
number of bits



In order to convert correctly **std_logic_vector** to **Integer** use descending index in the **std_logic_vector** and 0 for the rightmost index!

The integer type

- The usage of **Integer** to hold signals is generally **not recommended** for the same reason as the usage of **bit** and **bit_vector**!

When converting **std_logic_vector** to **Integer** all values different from '0' and '1' are lost, all undefined values are converted to the nice value '0'!

- Except in simulations, **always specify** the **range** of the **integer**, otherwise 32 bit logic will be synthesised!

```
subtype my_uint5bit   is Integer range 0 to 31;
subtype my_uint0to25  is Integer range 0 to 25;
subtype my_uint3to25  is Integer range 3 to 25;
subtype my_int_3to25   is Integer range -3 to 25;
subtype my_int_32to25  is Integer range -32 to 25;
subtype my_int_33to25  is Integer range -33 to 25;
```

} 5 bit
} 6 bit
7 bit

- Note that an upper limit different from 2^N-1 and lower limit different from 0 and -2^N are useful **only for simulations** (to get error when out of range)
- For synthesis the limits are used **only** to get the number of the bits
- Lower limit > 0 is **ignored** for synthesis (is the same as 0)

Mathematical operations with `integers`

```
signal byte1, byte2, byte3, byte4, byte5, byte6 : Integer range 0 to 16#FF#;  
signal sint1, sint2, sint3, sint4, sint5, sint6 : Integer range -128 to 127;  
signal word1, word2, word3 : Integer range 0 to 16#FFFF#;  
signal intg : Integer range -2**15 to 2**15-1;
```

```
begin
```

```
    byte1 <= 20;
```

```
    sint1 <= -20;
```

```
    byte2 <= byte1 / 2;      -- = 10
```

```
    byte3 <= byte1 mod 3;    -- = 2
```

```
    byte4 <= byte1 rem 3;    -- = 2
```

```
    byte5 <= byte1 + byte2;  -- = 30
```

```
    byte6 <= byte1 - byte2;  -- = 10
```

```
    sint2 <= sint1 / 2;      -- = -10
```

```
    sint3 <= sint1 mod 3;    -- = 1
```

```
    sint4 <= sint1 rem 3;    -- = -2
```

```
    sint5 <= sint1 / 3;      -- = -6
```

```
    sint6 <= sint1 + byte2;  -- = -10
```

```
    word1 <= byte1**2;       -- = 400
```

```
    word2 <= sint1**2;       -- = 400
```

```
    word3 <= byte1*byte2;    -- = 200
```

```
    intg <= byte1*sint1;     -- = -400
```

> for positive numbers `mod` = `rem`

> for negative numbers `mod` $\neq$ `rem`

Note that multiplication is **expensive** in hardware, division, `mod` and `rem` are generally **not** supported for synthesis (except for divider 2^N)

Mathematical operations with `std_logic_vectors`

- Using appropriate library it is possible to mix different types in mathematical operations and to apply mathematical operations (+ or -) to non-integer objects

```
USE IEEE.STD_LOGIC_ARITH.all;  
USE IEEE.STD_LOGIC_UNSIGNED.all;  
...  
signal data11b, data_inc : std_logic_vector(10 downto 0);  
...  
data_inc <= data11b + 1;  
If data11b is "1111111111" (2047), the result will be 0!
```

- The same is possible with the multiplication, but be careful, the multipliers are large! Use only for power of 2!
- For synthesis the division is supported only for power of 2, in this case it is just a shift (arithmetical or logical?)
- For every technology there are libraries with optimized modules for mathematical operations

The arithmetic packages(1)

- If you have only signed or only unsigned in the **entity** then you can use arithmetic operations with **std_logic_vector** by including the packages:

```
USE IEEE.STD_LOGIC_ARITH.all;
```

interpret **std_logic_vector** in
arithmetic operations as **signed**

```
USE IEEE.STD_LOGIC_SIGNED.all;
```

```
USE IEEE.STD_LOGIC_UNSIGNED.all;
```

only one
of them!

interpret **std_logic_vector** in
arithmetic operations as **unsigned**

```
USE IEEE.Numeric_Std_Signed.all;
```

```
USE IEEE.Numeric_Std_Unsigned.all;
```

VHDL-2008

The arithmetic packages(2)

- The better way is to use only:

```
USE IEEE.Numeric_Std.all;
```

- Declare as **signed** or **unsigned** all **std_logic_vectors** in the design, used in arithmetic operations :

```
signal uns : unsigned(7 downto 0);  
signal sgn : signed(7 downto 0);
```


- Note that the definition of **signed** and **unsigned** is exactly the same as of the **std_logic_vector**, but they are different and cannot be freely mixed (see the adder example)

Adder

```
LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;
USE IEEE.STD_LOGIC_UNSIGNED.all;
entity adder is
generic (N : Natural := 8);
port (
    cin : in  std_logic;
    a    : in  std_logic_vector(N-1 downto 0);
    b    : in  std_logic_vector(N-1 downto 0);
    cout : out std_logic;
    y    : out std_logic_vector(N-1 downto 0));
end adder;
architecture behav of adder is
signal sum : std_logic_vector(N downto 0);
begin
    sum <= cin + ('0' & a) + ('0' & b);
    y   <= sum(y'range);
    cout <= sum(sum'high);
end;
```

There are two possibilities:

 1. inferring (the synthesis tools recognize the adder and instantiate it from a library)
2. instantiating a ready adder component



Adder with `std_logic_arith`

```
LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;
USE IEEE.STD_LOGIC_ARITH.all;
entity adder is
generic (N : Natural := 8);
port (cin  : in  std_logic;
      a    : in  std_logic_vector(N-1 downto 0);
      b    : in  std_logic_vector(N-1 downto 0);
      cout : out std_logic;
      y    : out std_logic_vector(N-1 downto 0) );
end adder;
architecture a of adder is
signal sum : unsigned(N downto 0);
begin
    sum <= cin + unsigned('0' & a) + unsigned('0' & b);
    y   <= std_logic_vector(sum(y'range));
    cout <= sum(sum'high);
end;
```

Look at the source code of the packages `std_logic_arith`, `std_logic_signed` and `std_logic_unsigned` to learn more!

convert the `std_logic_vector` to `unsigned`




The diagram consists of two arrows. One arrow originates from the text 'convert the std_logic_vector to unsigned' and points to the `unsigned('0' & a)` term in the VHDL code. The second arrow originates from the same text and points to the `unsigned('0' & b)` term in the same line of code.

convert back from `unsigned` to `std_logic_vector`



The diagram consists of a single arrow pointing from the text 'convert back from unsigned to std_logic_vector' to the `std_logic_vector(sum(y'range))` term in the VHDL code.

Adders and parentheses

 


```

a : in  std_logic_vector(7 downto 0) ;
b : in  std_logic_vector(7 downto 0) ;
c : in  std_logic_vector(7 downto 0) ;
d : in  std_logic_vector(7 downto 0) ;
y : out std_logic_vector(7 downto 0) ;

```

`y <= a + b + c + d;`

 This implementation doesn't have the best timing, if all inputs are valid simultaneously



`y <= (a + b) + (c + d);`

Using parentheses one can force the structure to another tree of adders with better timing

Package description

```
library ieee;  
use ieee.std_logic_1164.all;
```

The package can be used for
declarations common to the project

```
package <package_name> is
```

```
constant <constant_name> : <type> := <value>;
```

```
subtype <vec_name> is std_logic_vector(<range>);
```

```
subtype <int_name> is Integer range <range>;
```

```
type ...;
```

```
...
```

```
function <func_name>(<var_name> : <var_type>;  
                    ...) return <ret_type>;
```

```
...
```

```
end <package_name>;
```

constant, type,
subtype, function,
procedure
declarations

```
package body <package_name> is
```

not visible outside

```
-- local constant, type, subtype declarations
```

```
-- function and procedure definitions
```

```
end <package_name>;
```

Function

```
library ieee;
use ieee.std_logic_1164.all;
```

The function can be used for some calculations

```
package <package_name> is
```

```
...
```

```
function <func_name>( <var1_name> : <var1_type>;
                    ...
                    <varN_name> : <varN_type>)
```

input variables

```
    return <ret_type>;
```

```
...
```

```
end <package_name>;
```

```
package body <package_name> is
```

```
function <func_name>(
    <var_name> : <var_type>;
    ...) return <ret_type> is
variable <var_name> : <var_type>;
```

the **functions** can use only **variables** but no **signals**!

```
begin
```

```
...
```

```
return <ret_value>;
```

```
end <func_name>;
```

```
...
```

```
end <package_name>;
```

use here everything what is typical for a **process** like **case**, **if**; timing statements are not allowed here!

the return value, of the <ret_type>

package
variable
function
loop
high
length

Package and function example

```
library ieee;
use ieee.std_logic_1164.all;
package mypack is
    constant ten : std_logic_vector(3 downto 0) := "1010";
    subtype my_data is std_logic_vector(10 downto 0);
    function se( src : std_logic_vector;
                ndst : Integer) return std_logic_vector;
end mypack;

package body mypack is

    function se( src : std_logic_vector;
                ndst : Integer) return
        std_logic_vector is
        variable tmp :
            std_logic_vector(ndst-1 downto 0);
        begin
            if src'length <= ndst then
                for i in src'range loop
                    tmp(i) := src(i);
                end loop;
            else
                for i in src'high+1 to ndst-1 loop
                    tmp(i) := src(src'high);
                end loop;
            else
                for i in 0 to ndst-1 loop
                    tmp(i) := src(i);
                end loop;
            end if;
            return tmp;
        end se;
    end mypack;
```

constant, type, function definitions

attribute

attribute

note the different symbol:
:= for variables
<= for signals

Operator overloading(1)

- VHDL is strictly typed language, so a function with the same name can be defined for different types of the arguments and of the result, the compiler automatically selects the proper one
- The operators like +, - can be overloaded with functions, here is a part of the `std_logic_arith` package:

```
...  
function "+" (L: UNSIGNED; R: UNSIGNED) return UNSIGNED;  
function "+" (L: SIGNED; R: SIGNED) return SIGNED;  
function "+" (L: UNSIGNED; R: SIGNED) return SIGNED;  
function "+" (L: SIGNED; R: UNSIGNED) return SIGNED;  
function "+" (L: UNSIGNED; R: INTEGER) return UNSIGNED;  
function "+" (L: INTEGER; R: UNSIGNED) return UNSIGNED;  
function "+" (L: SIGNED; R: INTEGER) return SIGNED;  
...
```

Operator overloading(2)

```

...
entity gate_vect is
generic (N : Natural := 4);
port (a : in std_logic_vector(N-1 downto 0);
      g : in std_logic;
      y : out std_logic_vector(N-1 downto 0) );
end gate_vect;
architecture ...
function "and" (L: std_logic; R: std_logic_vector)
  return std_logic_vector is
  variable tmp : std_logic_vector(R'range);
begin
  for i in R'range loop
    tmp(i) := R(i) and L;
  end loop;
  return tmp;
end;
function "and" (L: std_logic_vector; R: std_logic)
  return std_logic_vector is
begin
  return R and L;
end;
begin
  y <= g and a;
  y <= a and g;
...


```

In VHDL-2008 already there

unconstraint

left and right operand

both possible

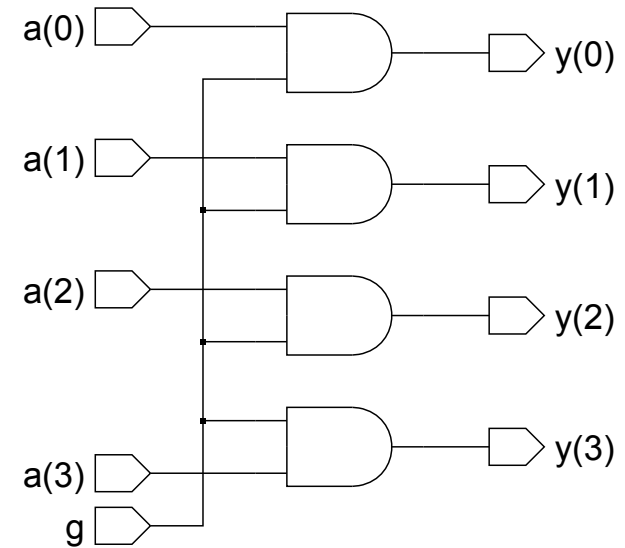

Such overloading functions can be put in a package, but be careful, your code will be not very standard - difficult to understand by other designers!

Library and package declarations

```
library library_name;
```

declare the **library** name

```
use library_name.package_name.all;
```

one **library** can contain many different **packages**


```
use library_name.otherpackage_name.all;
```

typically one uses the whole **package**, which stays in **all**

```
library work;
```

```
use work.my_package.all;
```

 the **library** work is by default always accessible, therefore this declaration is not necessary



typically here come the own **packages** with **constants**, **types**, **functions** and **procedures** used in the whole project

Package usage example

The **library** IEEE and the package **STD_LOGIC_1164** are typically always used

```
LIBRARY IEEE;  
USE IEEE.STD_LOGIC_1164.ALL;
```

```
use work.mypack.all; ← package
```


```
entity test_pack is  
  generic (Ni : Integer := 4);  
  port (se_in  : in  std_logic_vector(Ni-1 downto 0);  
        se_out : out my_data );  
end test_pack;
```

```
architecture a of test_pack is  
begin
```

```
  se_out <= se(se_in, se_out'length);  
end;
```

function from mypack

attribute

 

Variables

- Variable in a function
 - stores intermediate results of the calculations, exactly like in a normal computer program
- Variable in a process:
 - local for the process
 - holds its value between the activations of the process
 - the value assigned to it can be immediately used, like in a normal computer program

Example: signal vs. variable

```

signal sa : std_logic := 'X';
signal si : Integer range -7 to 7;
begin
process
variable va : std_logic;
variable vi : Integer range -7 to 7;
begin

```

act – actual value
sch – scheduled value } for the signals only!

	-- sa		si		va	vi
	-- act sch	act sch				
	-- 'X' -7				'U' -7	
sa <= '1';	-- 'X' 1	-7			'U' -7	
va := sa;	-- 'X' 1	-7			'X' -7	
si <= 0;	-- 'X' 1	-7	0		'X' -7	
vi := 0;	-- 'X' 1	-7	0		'X' 0	
wait for 10 ns;	-- 1	0			'X' 0	
va := '0';	-- 1	0			'0' 0	
si <= si + 1;	-- 1	0	1		'0' 0	
vi := vi + 1;	-- 1	0	1		'0' 1	
sa <= va;	-- 1 0	0	1		'0' 1	
si <= si + 1;	-- 1 0	0	1		'0' 1	
vi := vi + 1;	-- 1 0	0	1		'0' 2	
va := 'H';	-- 1 0	0	1		'H' 2	
si <= si + 1;	-- 1 0	0	1		'H' 2	
vi := vi + 1;	-- 1 0	0	1		'H' 3	
sa <= va;	-- 1 H	0	1		'H' 3	
si <= si + 1;	-- 1 H	0	1		'H' 3	
vi := vi + 1;	-- 1 H	0	1		'H' 4	
wait for 10 ns;	-- H	1			'H' 4	


the state after the execution of each line

the changes are marked with ●

for a **signal**: each new assignment overwrites the scheduled value, **wait** or **end process** updates the actual value

Barrel shifter right

 - Used to divide by power of 2
- Depending on the data type, the most significant bit filled with 0 or preserved
- First method, very simple description
- **A** size scalable, **shd** range not scalable



```
m <= ar_mode and A(A'high); -- the new MSB
with shd select
```

```
Y <= A
↑
output
```

when "000", ← shift shd

m & A(A'high downto 1) when "001", ←

m & m & A(A'high downto 2) when "010", ←

m & m & m & A(A'high downto 3) when "011", ←

m & m & m & m & A(A'high downto 4) when "100", ←

m & m & m & m & m & A(A'high downto 5) when "101", ←

m & m & m & m & m & m & A(A'high downto 6) when "110", ←

m & m & m & m & m & m & m & A(A'high downto 7) when "111", ←

(others => 'X') when others;



Area
1544 μm^2 (UMC 0.18 μm)
50 LUT4 (Altera ACEX 1k)
47 LUT4 (Xilinx Spartan 2E)

```

for ... loop
if...then...else
process

```

Barrel shifter – other methods

- Two attempts to write it more flexible

```

process(A, shd, m)
variable s : Integer;
variable tmp : std_logic_vector(Y'range);
begin

```



$t_D + 35\%$

```

    s := conv_integer(shd);
    tmp := A;
    for i in 0 to 7 loop
        if (i < s) then tmp := m & tmp(A'high downto 1); end if;
    end loop;

```

The variables are updated immediately!

```

    Y <= tmp;
end process;

```


copy the result to a signal, the variables are visible **only** locally in the **process**!

```

process(A, shd, m)
variable s : Integer;
begin
    s := conv_integer(shd);
    for i in Y'range loop
        if (i > (Y'high - s)) then Y(i) <= m;
        else Y(i) <= A(i+s); end if;
    end loop;
end process;

```

$t_D + 15\%$

 

= the simple solution from the previous page

Sy	- Synposys, UMC 0.18μm
LS	- Leonardo Spectrum, SLC 0.5 μm
Q	- Quartus, Altera ACEX 1K
X	- ISE, Xilinx

```

for ... loop
if...then...else
variable

```

Counting ones

Let's try to count the number of '1' in a N-bit vector. The process shown below can do this:


```

process(a)
variable nones : Integer range 0 to a'length;
begin
    nones := 0;
    for i in a'range loop
        if a(i)='1' then nones := nones + 1; end if;
    end loop;
    c <= conv_std_logic_vector(nones, c'length);
end process;

```

The variables are updated immediately!

copy the result to a signal

 

If the input is 15-bit, we can either use the **process** directly, or instantiate it 4 times for smaller pieces of the input vector and do the rest with adders. Which is better?

Recommendations

- Forget about how you write C programs!
- Here, the compiler synthesizes logic according to your code, working in parallel
- Write as simple as possible, without using complex constructs
- Do not write any line of code, without having some imagination of what kind of hardware will come out
- It is nice to write more universal and flexible, but not at the cost of design size and speed

The choice is yours!

- Never make anything simple and efficient when a way can be found to make it complex and wonderful (Murphy)

OR


- Perfection is achieved, not when there is nothing more to add, but when there is nothing left to take away (Antoine de Saint-Exupéry)

event
process
if ... then
elsif



Sequential circuits in VHDL - DFF

```
process(clk, rst_n)
begin
    if rst_n = '0' then q <= '0';
    elsif clk'event and clk='1' then
        q <= d;
    end if;
end process;
```

attribute

 

ASIC

  

Signal attributes

- **'event'** – true if an event occurred in the last simulation cycle
- For the very frequent conditions of edge sensitive flip-flops one can use the functions:

`clk'event and clk='1'` → `rising_edge(clk)` 
`clk'event and clk='0'` → `falling_edge(clk)` 

- **'last_value'** – actually the functions above use this attribute to exclude all clock transitions different from '0' → '1' (like 'x' → '1') or '1' → '0' (like 'u' → '0'):

`clk'event and clk='1' and clk'last_value='0'` 
`clk'event and clk='0' and clk'last_value='1'` 

- more signal attributes are available for simulation

Edge triggered **process** with one asynchronous set or reset

Unlike in a combinational process, list **here** only the ONE clock signal and the ONE reset signal, and no other signals read in the process!

```
process(<clock_signal>, <set_reset_signal>)
begin
    if <set_reset_signal> = <'0' | '1'> then
        ...
        asynchronous assignments of constants!
        ...
    elsif xxx_edge(<clock_signal>) then
        ...
        synchronous assignments
        ...
    end if;
end process;
```

! only one **elsif** without further
else checking for edge


Assigning values from other signals here is **not recommended** (see later **DFF with asynchronous load**)!

All output signals of the **process** must be here (see later **Shift register with bad reset**)

Unlike in the combinational case, the output signals of the **process** don't need to get values assigned in all cases – the circuit **has memory**!

Edge triggered process with synchronous set or reset

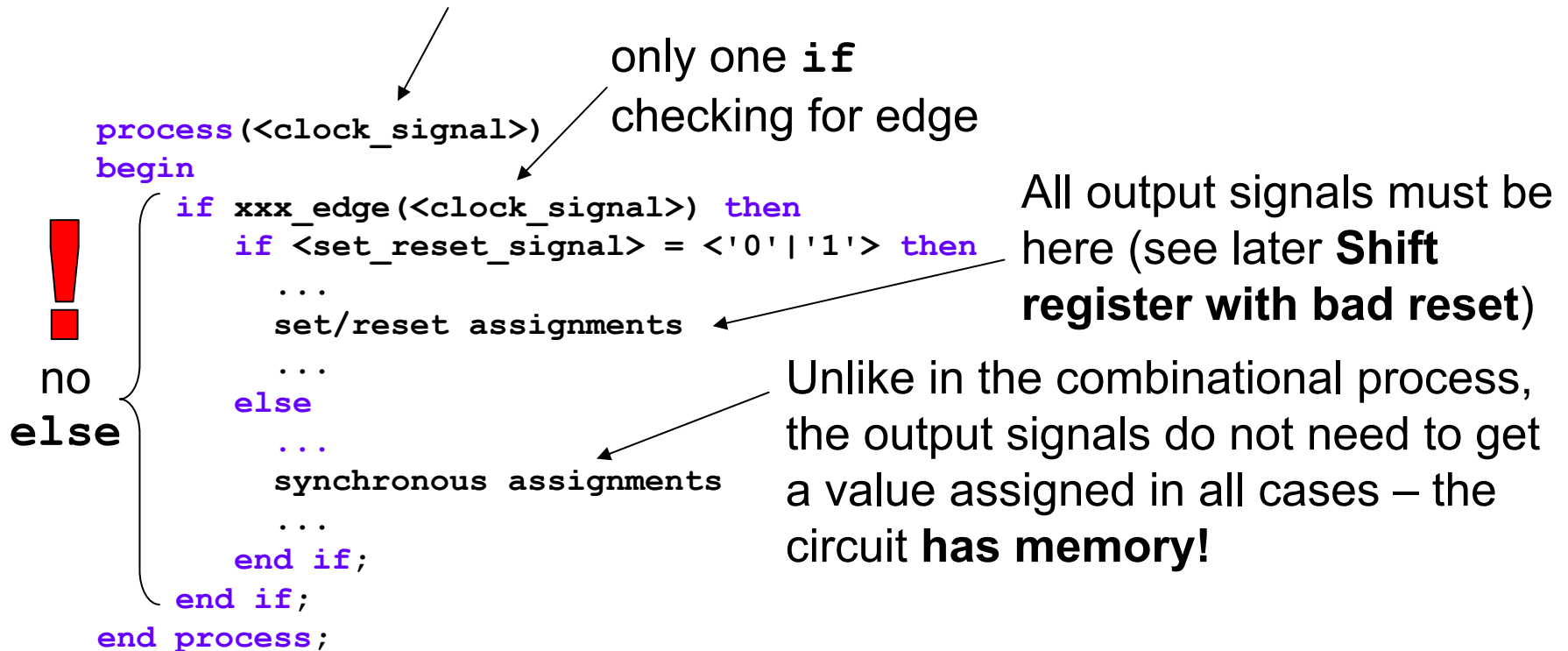Unlike in a combinational process, list **here** only the ONE clock signal and **no other** signals read in the process!



Sequential circuits in VHDL



DFFE(1)

event
process
— if ... then
elsif ... end if



```
process(clk, rst_n)
begin
    if rst_n = '0' then q <= '0';
    elsif clk'event and clk='1' then
        if en_n = '0' then
            q <= d;
        end if;
    end if;
end process;
```

  If DFF with enable is not available in the technology, it can be emulated with a DFF and a 2:1 mux:



DFF with enable(2)

```
process(clk, rst_n, en_n)
begin
    if rst_n='0' then
        q <= '0';
    elsif en_n = '0' and clk'event and clk='1' then
        q <= d;
    end if;
end process;
```



Altera Quartus 8.1

Error (10397): VHDL Event Expression error at my_dffe.vhd(57): can't form clock edge from S'EVENT by combining it with an expression that depends on a signal besides S

Leonardo Spectrum 2006b

...my_dffe.vhd",line 57: Error, clock expression should contain only one signal.

ISE 9.2 – no errors/warnings

! Not recommended descriptions !

```
process(clk, rst_n, en_n)
begin
    if rst_n = '0' then
        q <= '0';
    elsif en_n = '1' then NULL;
    else
        if clk'event and clk='1' then
            q <= d;
        end if;
    end if;
end process;
```



```
process(clk, rst_n, en_n)
begin
    if rst_n = '0' then
        q <= '0';
    elsif en_n = '0' then
        if clk'event and clk='1' then
            q <= d;
        end if;
    end if;
end process;
```



If missing


Altera Quartus 8.1:
Warning (10492): VHDL Process Statement warning at my_dffe.vhd(34): signal "en_n" is read inside the Process Statement but isn't in the Process Statement's sensitivity list

Leonardo Spectrum:
"my_dffe.vhd",line 45: Warning, en_n should be declared on the sensitivity list of the process.

Xilinx ISE 9.2:
WARNING:Xst:819 -
"my_dffe.vhd" line 30: The following signals are missing in the process sensitivity list:

A strange DFFE with "asynchronous clear"
 
```
process(clk, aclr_n)
begin
  if aclr_n = '0' then
    q <= '0';
  else
    q <= q_i;
  end if;
  if clk'event and clk='1' then
    if e = '1' then
      q_i <= d;
    else
      q_i <= q_i;
    end if;
  end if;
end process;
```



DFFE and TFF with procedure and process



```

procedure myreg(
  signal din  : in    std_logic;
  signal cpy  : in    std_logic;
  signal tgl  : inout std_logic;
  signal dout : out   std_logic) is


```

} similar to the ports
of an entity

```

begin
  if cpy = '1' then
    dout <= din;
    tgl  <= not tgl;
  end if;
end;
signal tqi : std_logic;
begin
process(clk)
begin
  if clk'event and clk='1' then
Or  myreg(d, ena, tqi, q);
    myreg(din => d, cpy => ena,
      tgl => tqi, dout => q);
  end if;
end process;
tq <= tqi;

```

 


call the procedure, like
instantiation of a component

DFFE and MUX with procedure

```

procedure mydff(
    signal din  : in  std_logic;
    signal clk  : in  std_logic;
    signal ena  : in  std_logic;
    signal q    : out std_logic) is
begin
    if rising_edge(clk) then
        if ena='1' then q <= din; end if;
    end if;
end;
...
mydff(din => d, ena => ena, clk => clk, q => q);

```

 


It is much better
to put such code
in entities and to
instantiate as
components!

```


procedure my21mux(
    signal a0  : in  std_logic_vector;
    signal a1  : in  std_logic_vector;
    signal sel  : in  std_logic;
    signal y    : out std_logic_vector) is
begin
    if sel = '1' then y <= a1;
    else y <= a0; end if;
end;

```

unconstraint 

 


the two differences

 

Latch is transparent

DFF or Latch (2) ? 🙄

 

```
process(clk, rst)
begin
  if rst = '1' then
    qpr <= '0';
  elsif clk='1' then
    qpr <= dpr;
  end if;
end process;
```

LATCH

```
process(clk)
begin
  if clk='1' then
    qp <= dp;
  end if;
end process;
```


?

```
process
begin
  wait until clk='1';
  qw <= dw;
end process;
```

DFF

The same VHDL code synthesized with 6 different tools and simulated (next slides)

DFF or Latch (3) ? 🙄

 

```
process(clk, rst)
begin
  if rst = '1' then
    qpr <= '0';
  elsif clk='1' then
    qpr <= dpr;
  end if;
end process;
```


LATCH
(with warnings)

```
process(clk)
begin
  if clk='1' then
    qp <= dp;
  end if;
end process;
```

```
process
begin
  wait until clk='1';
  qw <= dw;
end process;
```

DFF

DFF or Latch (4) ?

 

```
process(clk, rst)
begin
  if rst = '1' then
    qpr <= '0';
  elsif clk='1' then
    qpr <= d;
  end if;
end process;
```

```
process(clk)
begin
  if clk='1' then
    qp <= d;
  end if;
end process;
```

```
process
begin
  wait until clk='1';
  qw <= d;
end process;
```

```
process(clk, d)
begin
  if clk='1' then
    ql <= d;
  end if;
end process;
```

Not recommended!



As expected, in the **functional simulation** (ModelSim and Aldec AHDL) all **3 processes** behave as **edge triggered DFFs**! But 6 different synthesis tools found 1 or 2 latches! The fourth process on this page is a **latch** and is used for reference in the waveform.

```

process
  if ... then ...
  elsif ... else
  end if

```

Unwanted Latch

  


```

process(sel, d)
begin
  if    sel = "00" then y <= d(0);
  elsif sel = "01" then y <= d(1);
  elsif sel = "10" then y <= d(2);
  else
    y <= '-';
  end if;
end process;

```

 If the output is not specified for all possible inputs, Latches are inferred!



y preserves its last value when sel goes to "11"



How to avoid unwanted Latches?

- Anyway using latches is not recommended, except in some special cases
- Unwanted latches increase the size of the circuit, make the timing analysis more difficult (static timing analysis)
- All compilers assert warnings when finding a latch
 - The problem is, sometimes the warnings are so many and it is hard to read all of them
- In order to avoid latches in combinational circuits:
 - initialize the output signal at the beginning of the process, '–' is in many cases a good choice
 - use **case** instead of **if-then-else**, when you have non-priority choice, but this doesn't automatically prevent latches
- The synthesis tools don't interpret correctly the sensitivity lists, use only widely accepted descriptions of DFFs!

Combinational loop(1)

Latches are inferred when a feedback is detected by the synthesis tool. Here the problem is not only the latch itself, the feedback brings the circuit to oscillations.
  
```
process(a, sum, enable, clr_n)
begin
  if clr_n = '0' then
    sum <= (others => '0');
  elsif enable='1' then
    sum <= sum + a;
  end if;
end process;
s <= sum;
```




Combinational loop(2)


This should be a counter modulo 3. Its states are "00", "01", "10". The counter enters for short time the state "11", but then a reset pulse is generated.

```

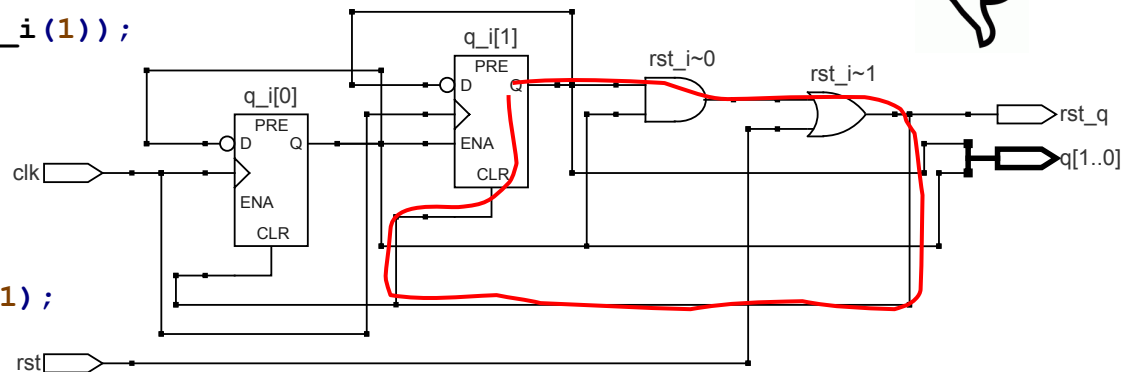rst_i <= rst or (q_i(0) and q_i(1));
process(clk, rst_i)
begin
    if rst_i = '1' then
        q_i <= "00";
    elsif rising_edge(clk) then
        q_i(0) <= not q_i(0);
        q_i(1) <= q_i(0) xor q_i(1);
    end if;
end process;
q <= q_i;
rst_q <= rst_i;
    
```



 
...more about this example in "Timing simulations"




Combinational loop(3)

There are several problems with this circuit:


- There are two combinational loops - each starts from a DFF output, goes through the AND and OR gates and closes to the reset port of the same DFF
- The duration of the reset pulse is probably on the lower limit, it could happen (depending on the supply voltage and temperature), that only one of the DFFs is cleared successfully
- It could happen, that after "00" and "01" when going to "10", both DFFs are for short time high, which leads to a reset pulse with very short duration
- The timing analysis is hard to be done
- The combinational logic has less than the usual complete period after an asynchronous reset, setup time violation is possible

 

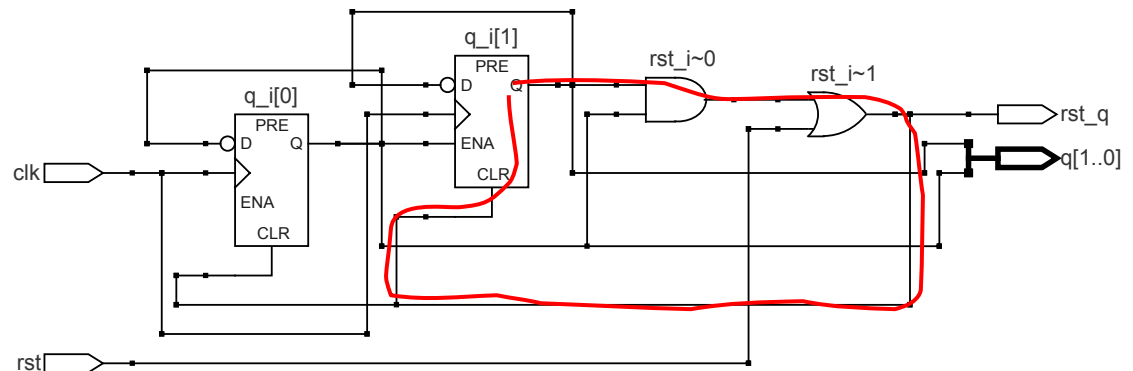
...more for this example in
"Timing simulations"



DFF with asynchronous set and reset

 
 
```
process(clk, pre, clr)
begin
    if pre = '1' and clr = '1' then
        q <= 'X';
    elsif clr = '1' then
        q <= '0';
    elsif pre = '1' then
        q <= '1';
    elsif clk'event and clk='1' then
        q <= d;
    end if;
end process;
```



Not a good idea to use both **pre** and **clr**:

- small additional delays and glitches can make the behaviour non-deterministic

DFF with asynchronous load



Not a good idea:

- additional logic resources
- difficult to fulfil timing conditions (**ad** must be valid when **aload** goes inactive)


```
process(clk, aload, ad)
begin
    if aload = '1' then
        q <= ad;
    elsif clk'event and clk='1' then
        q <= d;
    end if;
end process;
```



  When taking only **ad** and **aload** signals into account, this is a pure latch



Shift register with variables

 


For a **variable**, the VHDL code in the **process** is interpreted exactly like in a normal computer program, each assignment is immediate! For a **signal** the last value assigned is copied to it at the **end** of the **process**!

```
process (clk)
  variable a,b,c : std_logic;
begin
  if clk'event and clk='1' then
    a := d;
    b := a;
    c := b;
  end if;
  q <= c;
end process;
```

Wrong order!

correct!

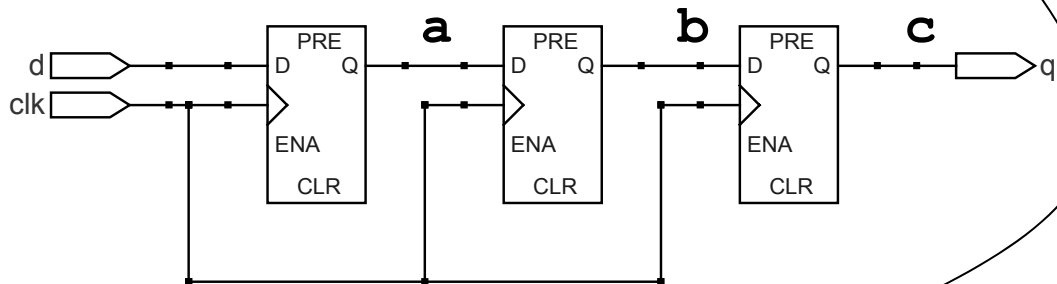



If using **signals** instead of **variables**, the order of the three lines is **not** important! Avoid using **variables** for real signals!

A simple counter with synchronous reset & load

```

signal q_i      : std_logic_vector(q'range);
constant full   : std_logic_vector(q'range) := (others => '1');
begin
process (clk)
begin
    if clk'event and clk='1' then
        if rst_n = '0' then
            q_i <= (others => '0');
        elsif sload = '1' then
            q_i <= d;
        elsif cnten = '1' then
            q_i <= q_i + 1;
        end if;
    end if;
end process;
q <= q_i;
co <= '1' when q_i = full and sload = '0' and cnten = '1' else '0';

```

  

Counter with signal/variable and std_logic_vector(1)

```

LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;
USE IEEE.STD_LOGIC_UNSIGNED.all;
entity counter_var is
generic (N : Natural := 8);
port (
    clk      : in  std_logic;
    rst_n    : in  std_logic;
    cnten     : in  std_logic;
    qss       : out std_logic_vector(N-1 downto 0);
    qsv       : out std_logic_vector(N-1 downto 0));

```

```

end counter_var;
architecture a of counter_var is
signal cntss : std_logic_vector(qss'range);
begin

```

-- using std_logic signal

```

process(clk, rst_n)
begin
    if rst_n = '0' then
        cntss <= (others => '0');
    elsif clk'event and clk='1' then
        if cnten = '1' then
            cntss <= cntss + 1;
        end if;
    end if;
end process;
qss <= cntss;

```



-- using std_logic variable

```

process(clk, rst_n)
variable cntsv : std_logic_vector(qsv'range);
begin
    if rst_n = '0' then
        cntsv := (others => '0');
    elsif clk'event and clk='1' then
        if cnten = '1' then
            cntsv := cntsv + 1;
        end if;
    end if;
    qsv <= cntsv;
end process;

```



Overflow
here is
ignored!

Both descriptions are equivalent.

In the case of **variable** be careful where to copy the value of the **variable** to the **signal**!

?

  Counter with signal/variable and std_logic_vector(2)



Wrong position of **this** line! The result is twice more DFFs and strange behaviour!

```
process(clk, rst_n)
    variable cntsv : std_logic_vector(qsv'range);
    begin
        if rst_n = '0' then
            cntsv := (others => '0');
        elsif clk'event and clk='1' then
            if cnten = '1' then cntsv := cntsv + 1; end if;
            qsv <= cntsv;
        end if;
    end process;
```



Counter with signal/variable and Integer(1)

```
entity counter_var is
generic (N : Natural := 8);
port (clk      : in  std_logic;
      rst_n    : in  std_logic;
      cnten    : in  std_logic;
      qis      : out std_logic_vector(N-1 downto 0);
      qiv      : out std_logic_vector(N-1 downto 0) );
end counter_var;
...
subtype counter_int is Integer range 0 to 2**N-1;
```


```
signal cntis : counter_int;
...
process(clk, rst_n)
begin
  if rst_n = '0' then
    cntis <= 0;
  elsif clk'event and clk='1' then
    if cnten = '1' then
      if cntis = counter_int'high then
        cntis <= 0;
      else
        cntis <= cntis + 1;
      end if;
    end if;
  end if;
end process;
qis <= conv_std_logic_vector(cntis, N);
```

```
-- using integer variable
process(clk, rst_n)
variable cntiv : counter_int;
begin
  if rst_n = '0' then
    cntiv := 0;
  elsif clk'event and clk='1' then
    if cnten = '1' then
      if cntiv = counter_int'high then
        cntiv := 0;
      else
        cntiv <= cntiv + 1;
      end if;
    end if;
  end if;
  qiv <= conv_std_logic_vector(cntiv, N);
end process;
```

Why ?
(next slide)

Counter with signal/variable and Integer(2)

 Writing simply `cntis <= cntis + 1;` leads to overflow error in the simulation




```

if cntis = counter_int'high then
    cntis <= 0;
else
    cntis <= cntis + 1;
end if;
    
```

Overflow here
is an error in
simulation!

 Some other synthesis tools do not introduce additional
logic, both descriptions are equivalent



```

cntis <= (cntis + 1) mod 2**N;
    
```

the better solution

Counter with signal/variable

```
signal cntss    : std_logic_vector(qss'range);
```

```
constant cntfull : std_logic_vector(qss'range) := (others => '1');
```

```
begin
```

```
process(clk, rst_n)
```

```
begin
```

```
  if rst_n = '0' then
    cntss <= (others => '0');
```

```
  elsif clk'event and clk='1' then
```

```
    if cnten = '1' then
```

```
      cntss <= cntss + 1;
```

```
      if cntss = cntfull then
```

```
        cntss <= (others => '0');
```

```
      end if;
```

```
    end if;
```

```
  end if;
```

```
end process;
```

```
qss <= cntss;
```

```
process(clk, rst_n)
```

```
variable cntsv : std_logic_vector(qsv'range);
```

```
begin
```

```
  if rst_n = '0' then
```

```
    cntsv := (others => '0');
```

```
  elsif clk'event and clk='1' then
```

```
    if cnten = '1' then
```

```
      cntsv := cntsv + 1;
```

```
      if cntsv = cntfull then
```

```
        cntsv := (others => '0');
```


```
      end if;
```

```
    end if;
```

```
  end if;
```

```
qsv <= cntsv;
```

```
end process;
```

 



Where comes the difference from?

Shift register with bad reset

```

process(clk, rst_n)
begin
    if rst_n = '0' then
        q <= '0';
    elsif clk'event and clk='1' then
        if en_n = '0' then
            q <= c;
            b <= a;
            a <= d;
            c <= b;
        end if;
    end if;
end process;
    
```

 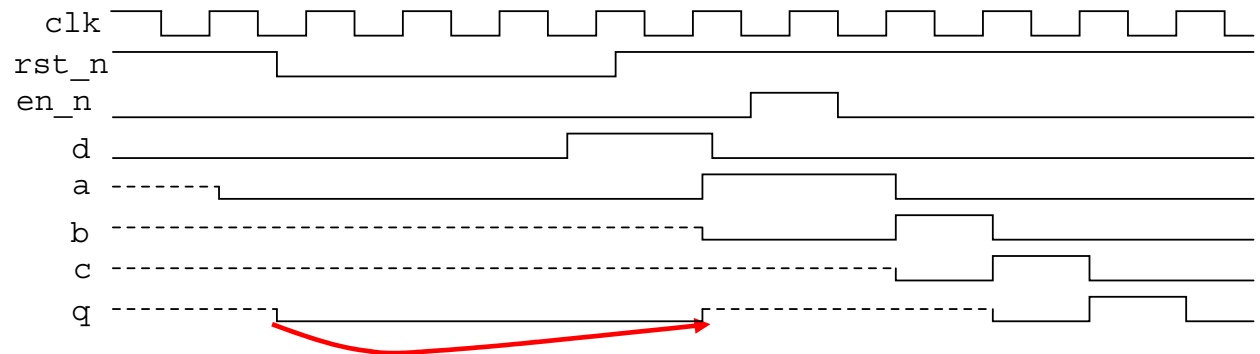If any register is missing in the reset part of the **process**, additional logic is inserted and the reset is impossible!




Shift register – correct reset 👍

```


process(clk, rst_n)
begin
  if rst_n = '0' then
    q <= '0'; a <= '0'; b <= '0'; c <= '0'; ← either all or no reset!
  elsif clk'event and clk='1' then
    if en_n = '0' then
      a <= d;
      b <= a;
      c <= b;
      q <= c;
    end if;
  end if;
end process;

```

The order is not important

 


 What will happen if we use latches instead of DFFs?



Shift register with parallel load

 
```
entity shift_reg_full is
generic (N : Natural := 10);
port(
...
signal q : std_logic_vector(N-1 downto 0);
begin
process(clk, rst_n)
begin
if rst_n = '0' then q <= (others => '0');
elsif clk'event and clk='1' then
if load = '1' then q <= din;
elsif shift='1' then
q <= q(N-2 downto 0) & serin;
end if;
end if;
end process;
```



```


serout <= q(N-1);
dout   <= q;
end;
```

 Two modules, one sends serially (**serout**) to the other



Gray code and Gray counters(1)

 - In case of a N-bit binary counter the number of bits changed at each clock vary from 1 to N, e.g. 0111 → 1000 → 1001 ... 1111 → 0000
- This might be a problem when transferring the counts to another clock domain due to the slight differences of the timing of the different bits



Gray code and Gray counters(2)

- Hamming distance between two N-bit words is defined as the number of differences in all bit positions, e.g.

00101 and

10111

have Hamming distance of 2


- In the binary coding the hamming distance between two adjacent codes can be from 1 to N
- In the Gray coding the hamming distance between two adjacent codes is always 1
- Unfortunately the arithmetic operations in Gray code are not easy, but
- The conversion from binary to Gray and back is not so difficult

Gray code and Gray counters(3)

Binary	distance	Gray
0 0 0 0		0 0 0 0
0 0 0 1	> 1	0 0 0 1
0 0 1 0	> 2	0 0 1 1
0 0 1 1	> 1	0 0 1 0
0 1 0 0	> 3	0 1 1 0
0 1 0 1	> 1	0 1 1 1
0 1 1 0	> 2	0 1 0 1
0 1 1 1	> 1	0 1 0 0
1 0 0 0	> 4	1 1 0 0
1 0 0 1	> 1	1 1 0 1
1 0 1 0	> 2	1 1 1 1
1 0 1 1	> 1	1 1 1 0
1 1 0 0	> 3	1 0 1 0
1 1 0 1	> 1	1 0 1 1
1 1 1 0	> 2	1 0 0 1
1 1 1 1	> 1	1 0 0 0
0 0 0 0	> 4	0 0 0 0


How to generate the code?

N+1 N-bit Gray code

 

Typical example for recursion
 → good for software, but not for hardware implementation


Gray code and Gray counters(4)

 

Binary → Gray



```
...
gray <= '0' & bin(N-1 downto 1) xor bin;
...
```

Gray → binary

 

```
...
signal bin_i : std_logic_vector(gray'range);
begin
    bin_i(N-1) <= gray(N-1);
binc: for i in N-2 downto 0 generate
    bin_i(i) <= gray(i) xor bin_i(i+1);
end generate;
bin <= bin_i;
...
```


Gray code and Gray counters(5)

  


Counting asynchronous events(1)

- It is not very nice to have tens of clocks in a single chip
 - Many clock domains (trees)
 - The counter & register outputs are not synchronous to the system clock and can not be used directly
- It might be better to run the counters with the system clock and to enable each counter properly
- Provided the input frequency is not higher than the system clock, there is a very simple solution

Counting asynchronous events(2)

 


 
Edge detection – the pulse duration on the `CLK_A` input must be larger than the period of the `CLK`, even if the frequency of `CLK_A` is very low




Here the only requirement is that the input frequency is below the system clock `CLK`

Filter for noisy or slow signals(1)

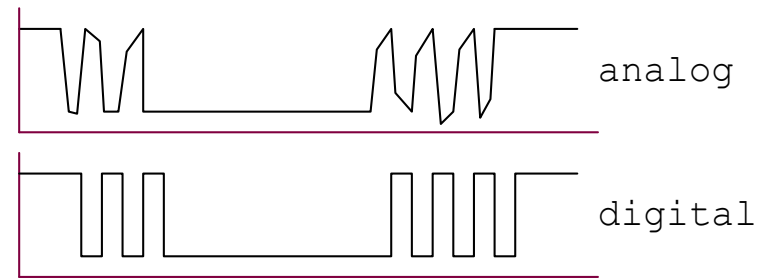 
- Some signals come from mechanical buttons and have many transitions



 
- or are very slow, compared to the typical digital signals



 One possible solution: low pass filter + Schmidt trigger with hysteresis



Filter for noisy or slow signals(2)

 

Filter for noisy or slow signals(3)


```
entity filt_short is
generic (N : Integer := 3);
port(clk  : in    std_logic;
      d    : in    std_logic;
      q    : out   std_logic);
end filt_short;
```

```
architecture a of filt_short is
signal samples : std_logic_vector(N-1 downto 0);
constant samples1 : std_logic_vector(N-1 downto 0) := (others => '1');
constant samples0 : std_logic_vector(N-1 downto 0) := (others => '0');
signal all_high, all_low_n, q_i : std_logic;
begin
  all_high <= '1' when samples = samples1 else '0';
  all_low_n <= '0' when samples = samples0 else '1';
  process(clk)
  begin
    if clk'event and clk='1' then
      samples <= samples(N-2 downto 0) & d;
      q_i <= (q_i or all_high) and all_low_n;
    end if;
  end process;
  q <= q_i;
end;
```

Using a shift register

The input is shifted in, the output is changed only if all bits in the shift register are equal

 The clock frequency must be low enough, for mechanical buttons in the order of 100Hz or below



Filter for noisy or slow signals(4)

entity filt_long is

generic (N : Integer := 3);

port(clk : in std_logic;

d : in std_logic;

q : out std_logic);

end filt_long;

architecture a of filt_long is

signal counts : Integer range 0 to N-2;

signal samples : std_logic_vector(1 downto 0);

begin

process(clk)

begin

if clk'event and clk='1' then

samples <= samples(0) & d;

if (samples(0) xor samples(1)) = '1' then -- different

counts <= N-2;

else

if counts = 0 then q <= samples(1);

else counts <= counts - 1; -- count down

end if;

end if;


end if;

end process;

end;

Using a counter


The input signal *d* must remain unchanged for *N* *clk* cycles in order to be copied to the output *q*, otherwise the counter will be reloaded

 




Sort4 – bubble sort

Lets try to sort 4 numbers in hardware. Maybe the simplest way is to first build a sorter for 2 numbers. Then combine many such blocks to realize something like a bubble sort.

```
entity sort2 is
generic(Nbits : Natural := 8; Nidx : Natural := 2);
port(
    dat0i : in  std_logic_vector(Nbits+Nidx-1 downto 0);
    dat1i : in  std_logic_vector(Nbits+Nidx-1 downto 0);
    dat0o : out std_logic_vector(Nbits+Nidx-1 downto 0);
    dat1o : out std_logic_vector(Nbits+Nidx-1 downto 0));
end sort2;
architecture a of sort2 is
    signal d0gtd1 : std_logic;
    signal dat0cmp, dat1cmp : std_logic_vector(Nbits-1 downto 0);
begin
    dat0cmp <= dat0i(Nbits+Nidx-1 downto Nidx);
    dat1cmp <= dat1i(Nbits+Nidx-1 downto Nidx);
    d0gtd1  <= '1' when dat0cmp > dat1cmp else '0';
    dat0o   <= dat0i when d0gtd1 = '1' else dat1i;
    dat1o   <= dat1i when d0gtd1 = '1' else dat0i;
end;
```

 


Sort4 – some better architectures

   


Sort4 - pipelining

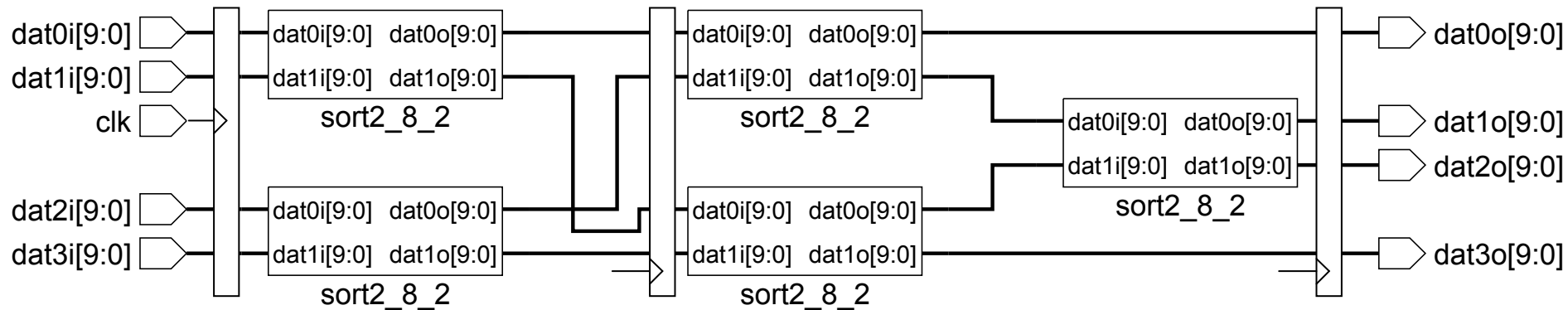In order to estimate easier the speed, we can first put registers at the input and at the output




The next natural step would be to put one register in the middle.
We pay with latency, but we get the design running faster (+56%).

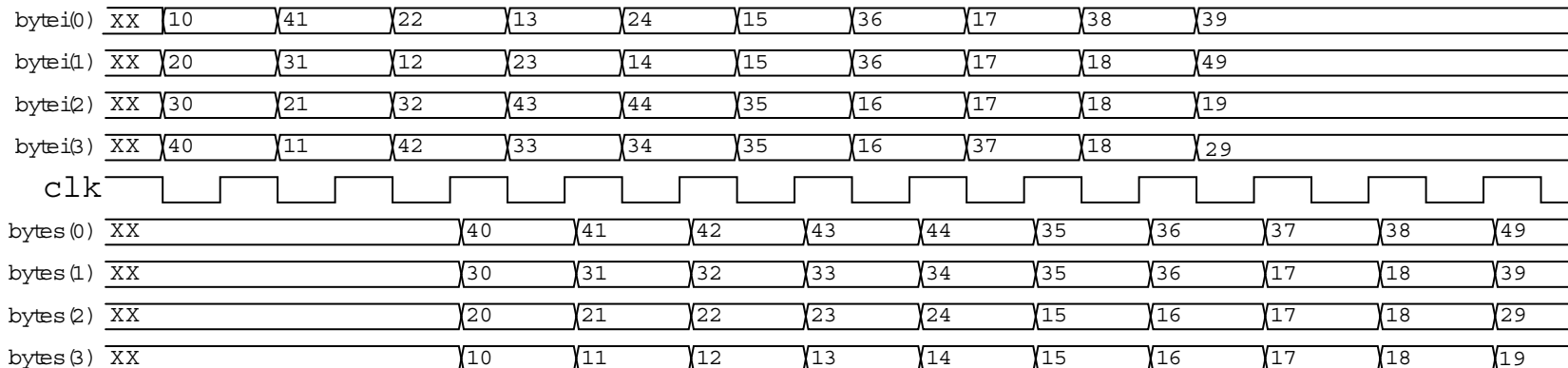

Sort4 – the best solution(1)

 Compare each pair, put the result (6 bits) into a LUT and calculate the select inputs of the 4 output mux



Same area as the bubble sort, but twice faster! Pipelining here is straightforward.

Sort4 – the best solution(2)

The LUT can be realized as a **process** with a big **case** (in total 24 cases, the rest are don't care). The generation of the VHDL **case** code can be done by a simple C++ program.

```
#include <iostream>
#include <iomanip>
using namespace std;
int pos(int p, int a, int b, int c, int d)
{
```

```
    if (a==p) return 0x00;
    if (b==p) return 0x01;
    if (c==p) return 0x10;
    if (d==p) return 0x11;
    return 0;
}
```

```
int main(void)
```

```
{
    int a,b,c,d;
    for(a=0; a<4; a++)
        for(b=0; b<4; b++)
            for(c=0; c<4; c++)
                for(d=0; d<4; d++)
                    if ((a!=b) && (b!=c) && (c!=d) && (a!=c) && (a!=d) && (b!=d))
                    {
```

```
                        cout<<"when " << " " << dec<<(a)<<(b)<<(c)<<(d)<<(d)<<(a)<<(a)<<(b)<<(c)<<"=" << " ";
                        cout<<"mux(0) <=" << " " << hex<<setw(2)<<setfill('0')<<pos(3,a,b,c,d)<<" " << " ";
                        . . .
                    }
```

The LUT 6 → 8 bit in VHDL

```
sel <= d0gt1 & d1gt2 & d2gt3 & d3gt0 & d0gt2 & d1gt3;
```

```
process(sel)
```

```
begin
```

```
    case sel is
```

```
        when "000100"=>mux(0)<="11";mux(1)<="10";mux(2)<="01";mux(3)<="00";
```

```
        when "001100"=>mux(0)<="10";mux(1)<="11";mux(2)<="01";mux(3)<="00";
```

```
        ...
```


```
        when others =>mux(0)<="--";mux(1)<="--";mux(2)<="--";mux(3)<="--";
```

```
    end case;
```

```
end process;
```

Sorting larger arrays - sort8

 How to extend the sort entity for larger N? For N=8 the simplest solution is shown below, using 5 x sort4 entities, 3 of them slightly simplified (2 of the 6 comparators in the modified sort2p2 are not necessary as the two input pairs are already sorted, the LUT becomes smaller)




Again, pipelining here is straightforward. Generally this approach can be used to double the N, the logic explodes by factor of 4 to 5.

Pseudorandom generators(1)


N-bit shift register with a feedback, used to generate pseudorandom numbers. Note that the number of possible states is $2^N - 1$, not 2^N !

The example below is for $N=4$.

 

```
di <= sr(3) xor sr(2); -- or psrg(sr)
process(clk, rst_n)
begin
    if rst_n = '0' then
        sr <= (others => '0');
        sr(0) <= '1';
    elsif clk'event and clk='1' then
        sr <= sr(sr'high-1 downto 0) & di;
    end if;
end process;
q <= sr;
```

(next slide)

 

Used: for built-in tests of memories; to generate input data in testbenches; for Monte Carlo simulations; as simple frequency divider

Pseudorandom generators(2)

```
function psrg(sr : std_logic_vector) return std_logic is
variable bit0 : std_logic;
begin
  case sr'length is
    when 32 => bit0 := sr(31) xor sr(21) xor sr( 1) xor sr( 0);
    when 31 => bit0 := sr(30) xor sr(27);
    when 30 => bit0 := sr(29) xor sr( 5) xor sr( 3) xor sr( 0);
    when 29 => bit0 := sr(28) xor sr(26);
    when 28 => bit0 := sr(27) xor sr(24);
    when 27 => bit0 := sr(26) xor sr( 4) xor sr( 1) xor sr( 0);
    when 26 => bit0 := sr(25) xor sr( 5) xor sr( 1) xor sr( 0);
    when 25 => bit0 := sr(24) xor sr(21);
    when 24 => bit0 := sr(23) xor sr(22) xor sr(21) xor sr(16);
    when 23 => bit0 := sr(22) xor sr(17);
    when 22 => bit0 := sr(21) xor sr(20);
    when 21 => bit0 := sr(20) xor sr(18);
    when 20 => bit0 := sr(19) xor sr(16);
    when 19 => bit0 := sr(18) xor sr( 5) xor sr( 1) xor sr( 0);
    when 18 => bit0 := sr(17) xor sr(10);
    when 17 => bit0 := sr(16) xor sr(13);
    when 16 => bit0 := sr(15) xor sr(14) xor sr(12) xor sr( 3);
    when 14 => bit0 := sr(13) xor sr( 4) xor sr( 2) xor sr( 0);
    when 13 => bit0 := sr(12) xor sr( 3) xor sr( 2) xor sr( 0);
    when 12 => bit0 := sr(11) xor sr( 5) xor sr( 3) xor sr( 0);
    when 11 => bit0 := sr(10) xor sr( 8);
    when 10 => bit0 := sr( 9) xor sr( 6);
    when  9 => bit0 := sr( 8) xor sr( 4);
    when  8 => bit0 := sr( 7) xor sr( 5) xor sr( 4) xor sr( 3);
    when  5 => bit0 := sr( 4) xor sr( 2);
    when 15 | 7 | 6 | 4 | 3 =>
      bit0 := sr(sr'length-1) xor sr(sr'length-2);
    when others => bit0 := '-';
  end case;
  return bit0;
end;
```

The feedback expressions
for some sizes of the shift
register, based on:

Xilinx APP 052 July 7, 1996,
ver. 1.1
- table for n=3...168

The generator can not exit
the state "00...00"!

Registerfile


```

...
subtype reg_data is std_logic_vector(Nd-1 downto 0);
type rf_data_array is array(0 to 2**Na-1) of reg_data;
signal rf_data : rf_data_array;
signal we_i    : std_logic_vector(rf_data_array'range);
begin
  process(waddr, we) -- decoder with enable
  begin
    we_i <= (others => '0');
    we_i(conv_integer(waddr)) <= we;
  end process;
ri: for i in rf_data_array'range generate
  process(clk, rst_n) -- the registers
  begin
    if rst_n = '0' then rf_data(i) <= (others => '0');
    elsif clk'event and clk='1' then
      if we_i(i) = '1' then
        rf_data(i) <= din;
      end if;
    end if;
  end process;
end generate;
-- the two output mux
rdata <= rf_data(conv_integer(raddra));
rdatb <= rf_data(conv_integer(raddrb));
end;

```

As a part of a RISC
CPU core

 Number and size of
registers set through
generics



State machines

State machines

- Two or three process implementation
- One process implementation
- Registered outputs and latency
- State encoding, stability
- Possible timing problems
- Partitioning of large machines
- Error protection

State machines in VHDL (1)

```
type state_type is (S0, SL, SR, SA);
```

 ← enumerated type

```
signal present_st, next_st : state_type;
```

```
begin
```

```
process(present_st, L, R, W)
```

```
begin
```

```
    next_st <= present_st;
```

```
    case present_st is
```

```
    when S0 => if W = '1' then next_st <= SA;
```

```
                elsif L = '1' then next_st <= SL;
```

```
                elsif R = '1' then next_st <= SR;
```

```
            end if;
```

```
    when SL => if L = '0' and R = '1' then next_st <= SR;
```

```
                else next_st <= S0;
```

```
            end if;
```

```
    when SR => if L = '1' then next_st <= SL;
```

```
                else next_st <= S0;
```

```
            end if;
```

```
    when SA => next_st <= S0;
```

```
    --when others => ...
```

```
    end case;
```

```
end process;
```

Next state as a function of
the present state and the
inputs

when others is not necessary
in case of enumerated type

1st process

State machines in VHDL (2)

Register to store the current state

```
process(clk, rst_n)
begin
    if      rst_n = '0'                then present_st <= S0;
    elsif clk'event and clk='1' then present_st <= next_st;
    end if;
end process;
```

2nd process

Calculate the outputs as a function of the current state (Moore machine):


```
process(present_st)
begin
    LL <= '0'; LR <= '0';
    case present_st is
    when SL => LL <= '1';
    when SR => LR <= '1';
    when SA => LL <= '1'; LR <= '1';
    when others => NULL;
    end case;
end process;
```

3rd process

... or current state and inputs
(for Mealy machines)

This process can be combined
with the first one – two process
description

State machines in VHDL (3)

 

State machines in VHDL – one process description

```
process(clk, rst_n)
begin
```

```
    if rst_n = '0' then st_m <= S0;
    elsif clk'event and clk='1' then
        case st_m is
            when S0 => if W = '1' then st_m <= SA;
                       elsif L = '1' then st_m <= SL;
                       elsif R = '1' then st_m <= SR; end if;
            when SL => if L = '0' and W = '1' then st_m <= SR;
                       else st_m <= S0; end if;
            when SR => if L = '1' then st_m <= SL;
                       else st_m <= S0; end if;
            when SA => st_m <= S0;
            when others => st_m <= "XX";
        end case;
    end if;
```

Description in
one process only

this line depends on the encoding!

```
end process;
```

```
LL <= st_m(1); LR <= st_m(0);
```

The outputs are part of the state
coding in this example

- For small machines seems to be the shortest description
- Not recommended for large state machines!

State machines in VHDL – manual encoding

```
subtype state_type is std_logic_vector(1 downto 0);  
constant S0 : state_type := "00";  
constant SL : state_type := "10";  
constant SR : state_type := "01";  
constant SA : state_type := "11";  
signal present_st, next_st : state_type;
```

← This works always!

OR

```
type state_type is (S0, SL, SR, SA);  
attribute ENUM_ENCODING : STRING;  
attribute ENUM_ENCODING of state_type : type is "0001 0010 0100 1000";
```

 one-hot

OR

```
attribute ENUM_ENCODING of state_type : type is "00 01 10 11";
```

 binary

```
signal present_st, next_st : state_type;
```

The exact way to set the encoding in the VHDL code depends on the software tool used, this example is for ISE (Xilinx)

The encoding style can be set globally for all entities (tool specific)

State machines in VHDL - registered outputs

It is often better to have registered outputs of the state machine. The simplest way is shown below, but this adds latency:


```
process(clk, rst_n)
begin
    if rst_n = '0' then
        present_st <= S0; LL <= '0'; LR <= '0';
    elsif clk'event and clk='1' then
        present_st <= next_st;
        if present_st = SL or present_st = SA then LL <= '1';
                                                else LL <= '0'; end if;
        if present_st = SR or present_st = SA then LR <= '1';
                                                else LR <= '0'; end if;
    end if;
end process;
```

How to avoid this extra latency?

Use the `next_st` instead of the `present_st`:

```
if next_st = SL or next_st = SA then LL <= '1';
                                else LL <= '0'; end if;
if next_st = SR or next_st = SA then LR <= '1';
                                else LR <= '0'; end if;
```

 
State machines in VHDL – position decoder(1)



Note: CLK is enough faster than P1, 2

State machines in VHDL – position decoder(2)

 This is a good example how a Mealy type of machine can significantly reduce the number of the states



The outputs are active only while jumping to another state.

How many states are necessary for a Moore machine ?

State machines in VHDL – position decoder(3)

```
type state_type is (S00, S01, S11, S10);  
signal present_st, next_st : state_type;  
signal p1s, p2s : std_logic;  
...
```

```
process(present_st, p1s, p2s)  
begin
```

```
    EN <= '0'; UP <= '-'; -- the default is no counting
```

```
    next_st <= present_st;
```

```
    case present_st is
```

```
        when S00 => if    p1s = '1' then next_st <= S10; EN <= '1'; UP <= '0';  
                    elsif p2s = '1' then next_st <= S01; EN <= '1'; UP <= '1';  
                    end if;
```

```
        when S01 => if    p1s = '1' then next_st <= S11; EN <= '1'; UP <= '1';  
                    elsif p2s = '0' then next_st <= S00; EN <= '1'; UP <= '0';  
                    end if;
```

```
        when S11 => if    p1s = '0' then next_st <= S01; EN <= '1'; UP <= '0';  
                    elsif p2s = '0' then next_st <= S10; EN <= '1'; UP <= '1';  
                    end if;
```

```
        when S10 => if    p1s = '0' then next_st <= S00; EN <= '1'; UP <= '1';  
                    elsif p2s = '1' then next_st <= S11; EN <= '1'; UP <= '0';  
                    end if;
```

```
    end case;
```

```
end process;
```

this process calculates
the next state and the
outputs

State machines in VHDL – position decoder(4)


```
process(clk)
variable p12s : std_logic_vector(1 downto 0);
begin
    if clk'event and clk='1' then
        p1s <= P1; -- synchronize the inputs
        p2s <= P2; -- to the Mealy machine!
        p12s := p1s & p2s;
        if rst_n = '0' then -- jump to the correct state
            case p12s is
                when "00" => present_st <= S00;
                when "01" => present_st <= S01;
                when "10" => present_st <= S10;
                when "11" => present_st <= S11;
                when others => NULL;
            end case;
        else
            present_st <= next_st; -- store the next state
        end if;
    end if;
end process;
```

this is very important!


this is no register!

a somehow unusual reset,
asynchronous would be dirty

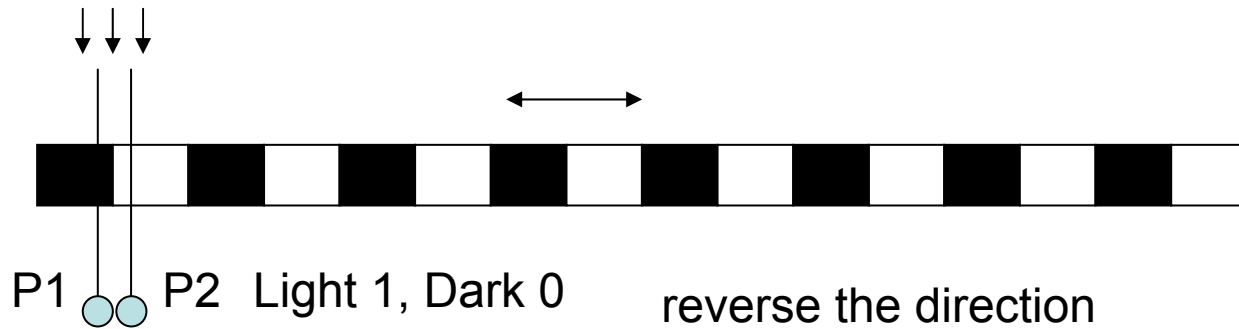State machines in VHDL – position decoder(5)



Simulation

 

State machine - encoding

- One-hot

- + fast decoding
- many illegal states

1	0	0	0	0
0	1	0	0	0
0	0	1	0	0
0	0	0	1	0
0	0	0	0	1

} 5 valid, 27 illegal combinations

- Binary, Gray

- + without or with only a few (< 50%) illegal states
- more complex decoding

- Using the outputs + eventually additional bits


- + Synchronous outputs
- + The decoding is not necessary
- Eventually more logic

0	0	0
0	0	1
0	1	0
0	1	1
1	0	0
1	0	1
1	1	0
1	1	1

State machine – illegal states

- In case of 5 states there are 32 possible states in one-hot and 8 in binary coding
- Depending on the realization of the next state logic, once entering an illegal state the state machine may never recover to a normal state
- The standard **when others => sm <= . . .** in the description of the state machine doesn't guarantee anything in most cases!
- Only when encoding the states manually, **when others =>** could help (or when activating **safe implementation** option in the synthesis software if available)
- How is it possible for a state machine to enter some wrong state? How to avoid this?


State machine – setup/hold

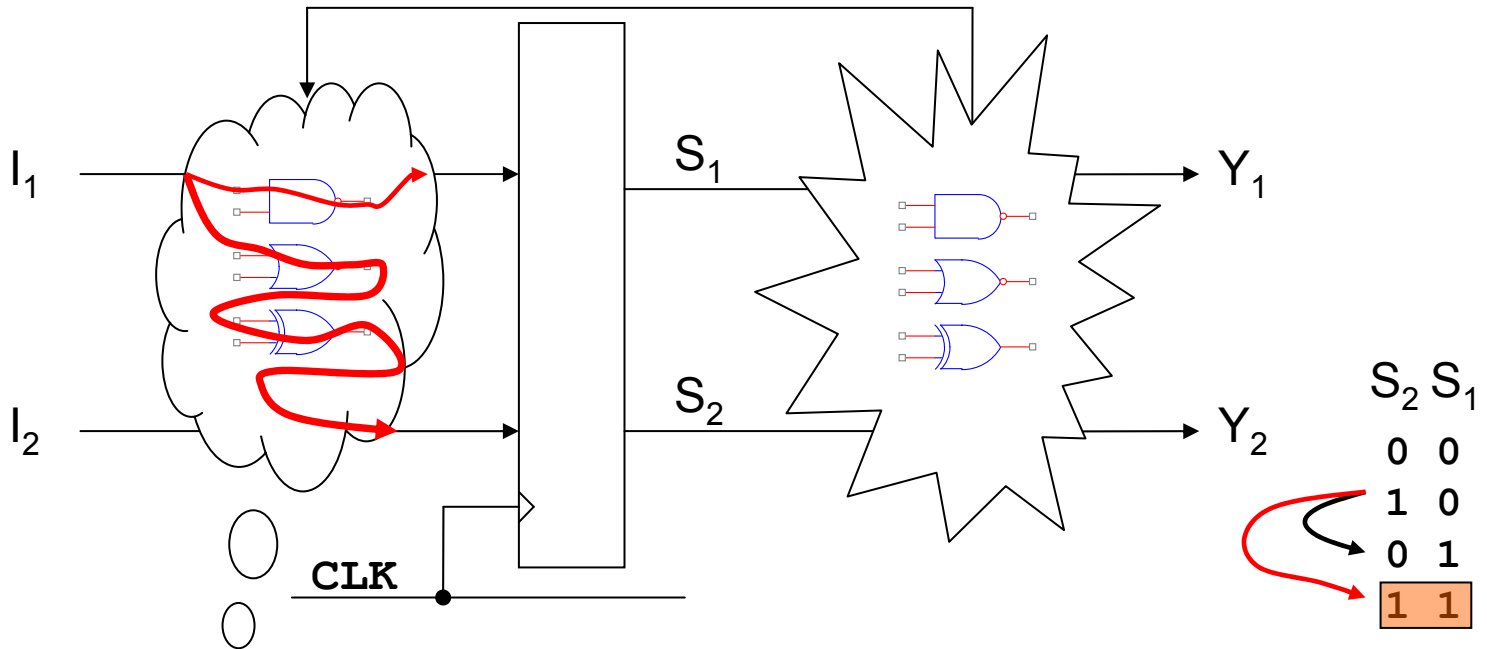

The propagation delays from the input I_1 to S_1 and S_2 are different. If the input signal is asynchronous to the CLK , it can happen that S_1 stores the new, but S_2 the old value, as a consequence the state machine jumps to a totally wrong state (different from the old and the next one), which could be one of the illegal states

→ **All inputs to a state machine must be synchronized to the CLK!!!**


Synchronize input signals

 

... before using them in the chip

General recommendation, not only for the inputs to the state machines

 
Due to the different delays, the input signal will be interpreted by a part of the chip as 1, by another part as 0



Partitioning of state machines (1)

- How to encode large state machines? E.g. with 33 states, then when using
 - one-hot encoding we need 33 bits and have about $8 \cdot 10^9$ unused states!
 - when using binary or Gray encoding we have 64 total states
 - Can we do something more?
- YES!
 - first try to minimize the number of the states
 - partition the state machine into several smaller

Partitioning of state machines (2)

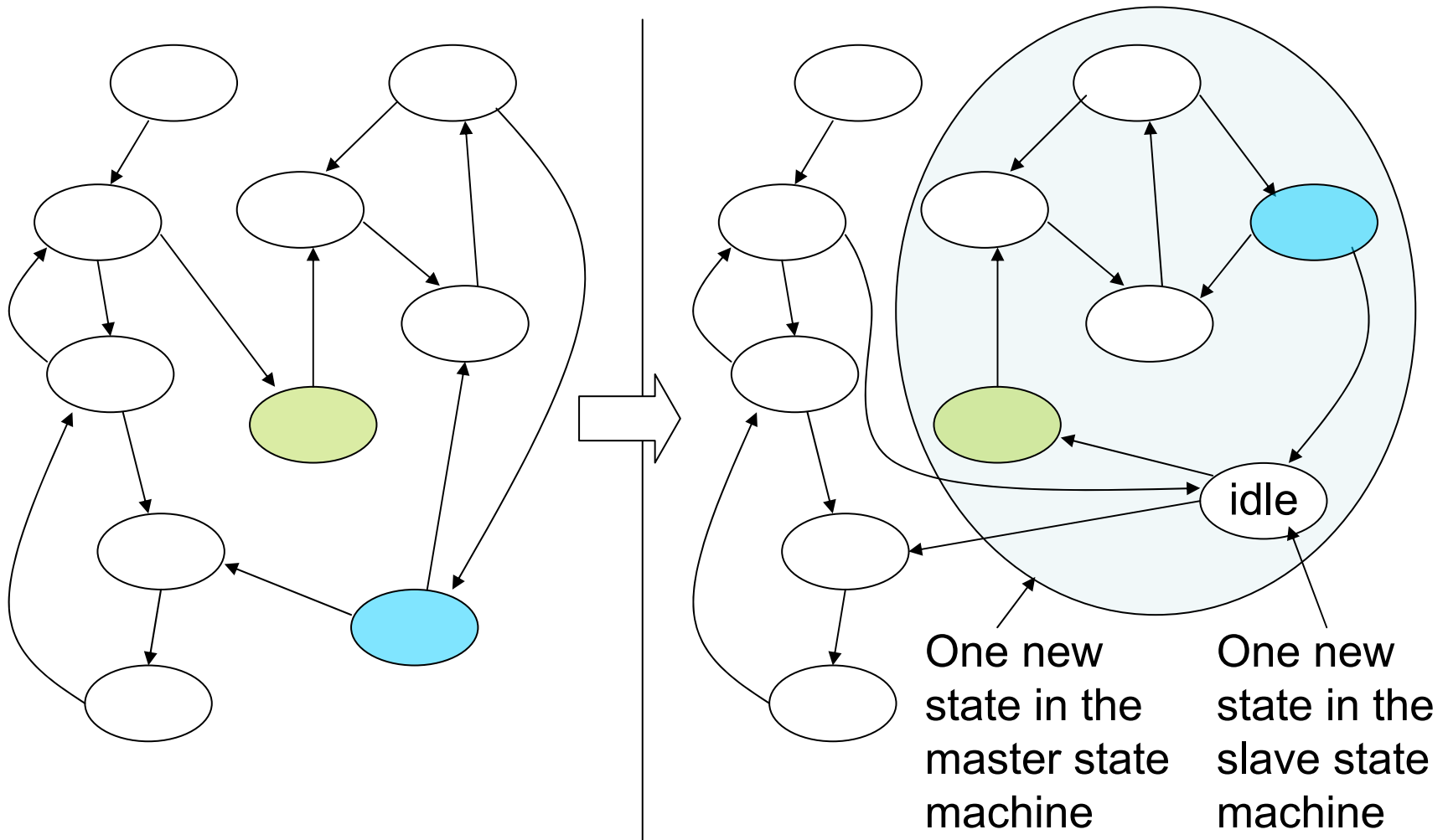

Partitioning of state machines

(3)

- Similar strategy as when partitioning a large design into several subdesigns (entities) – hierarchy!
- Try to find the independent (orthogonal) parts of the state machine with single transitions at the boundary
- Extract these parts as slave state machines, eventually put some additional states in the master and in the slave machines
- When the master reaches the entry state to the slave machine, it remains there until the slave has finished
- For the slave all other master states act as synchronous reset
- With some care the extra latency when making a transition from one to another machine can be avoided

Error protection (1)

- Because of electrical noise or ionizing radiation it is possible that single bits toggle
- With a Hamming-Code single bit errors can be corrected, by adding control bits to the data word (e.g. for 4 bits 3 control bits are needed, for 32 bits – 6)
- If the register holding the **state of a state machine** has additional Hamming control bits and the coding/decoding logic, a single bit flip in the state register will be corrected at the next clock

Error protection (2)

- The principle of operation of the Hamming-Code is simple:
 - The Hamming distance between two words is defined as the number of differences in all bit positions, e.g. **00101** and **10111** have Hamming distance of 2
 - The set of the possible data words is extended, but the valid data words remain a small subset, so that the min Hamming distance between any two valid words is e.g. 3
 - In case of one bit error the data word is corrected to the nearest valid data word
 - By increasing the distance, more detection/correction can be achieved

